

Solutions

ECE 120 Final Exam Spring 2016

Friday, May 13, 2016

Name:			NetID:		
Discussion Section:					
9:00 AM	<input type="checkbox"/>	AB1			
10:00 AM	<input type="checkbox"/>	AB2			
11:00 AM	<input type="checkbox"/>	AB3			
12:00 PM	<input type="checkbox"/>	AB4			
1:00 PM	<input type="checkbox"/>	AB5	<input type="checkbox"/>	ABA	
2:00 PM	<input type="checkbox"/>	AB6			
3:00 PM	<input type="checkbox"/>	AB7	<input type="checkbox"/>	ABB	
4:00 PM	<input type="checkbox"/>	AB8	<input type="checkbox"/>	ABC	
5:00 PM	<input type="checkbox"/>	AB9	<input type="checkbox"/>	ABD	

- Be sure that your exam booklet has 12 pages.
- Write your name, netid and check discussion section on the title page.
- Do not tear the exam booklet apart.
- Use backs of pages for scratch work if needed.
- This is a closed book exam. You may not use a calculator.
- You are allowed two handwritten 8.5 x 11" sheet of notes (both sides).
- Absolutely no interaction between students is allowed.
- Clearly indicate any assumptions that you make.
- The questions are not weighted equally. Budget your time accordingly.

Problem 1	16 points	_____
Problem 2	11 points	_____
Problem 3	19 points	_____
Problem 4	15 points	_____
Problem 5	22 points	_____
Problem 6	20 points	_____
Problem 7	22 points	_____

Total	125 points	_____
-------	------------	-------

Problem 1 (16 points): Binary Representation and Operations

1. (12 points) Suppose an **8-bit** processor performs **2's complement arithmetic addition and subtraction** and generates the following one-bit condition codes: **P** for *positive*, **N** for *negative*, **O** for *overflow*, and **C** for *carryout* bit. For each of the operations below, give the result of the operation (**in hexadecimal with correct number of digits**) as performed by this processor and give the value of the condition code bits (**in binary**) after the operation is complete.

Operation	Result of arithmetic operation (in hexadecimal)	P	N	O	C
10000000 - 00011011	x65	1	0	1	1
10101010 + 11101110	x98	0	1	0	1
11000101 + 00111011	x00	0	0	0	1

2. (4 points) Suppose a 24-bit instruction takes the following format:

OPCODE	DR	SR1	SR2	UNUSED
--------	----	-----	-----	--------

- a. If there are 40 opcodes and 24 registers, what is the **minimum** number of bits required to represent:

the opcodes? 6 bits

the source register 1 (SR1)? 5 bits

- b. What is the **maximum** number of UNUSED bits in this instruction encoding?

Answer: 3 bits

- c. If during a complete re-design of the ISA there are 3 times the number of opcodes we had before, how many **additional bits** would be required to represent the opcodes?

Answer: 1 additional bits

Problem 2 (11 points): Synchronous Counter

Using D flip-flops, design a 3-bit counter that counts in the following sequence: 1, 5, 2, 6, 7, 1 ...

1. (8 points) The current state of the counter is denoted by $S_2S_1S_0$. Fill in the K-maps for S_2^+ , S_1^+ and S_0^+ using don't cares whenever possible.

S_2^+		S_1S_0			
		00	01	11	10
S_2	0	x	1	x	1
	1	x	0	0	1

S_1^+		S_1S_0			
		00	01	11	10
S_2	0	x	0	x	1
	1	x	1	0	1

S_0^+		S_1S_0			
		00	01	11	10
S_2	0	x	1	x	0
	1	x	0	1	1

2. (3 points) Write **minimal SOP** Boolean expressions for S_2^+ , S_1^+ , and S_0^+ .

$$S_2^+ = \frac{\overline{S_0} + \overline{S_2}}{\quad}$$


$$S_1^+ = \frac{\overline{S_0} + S_2\overline{S_1}}{\quad}$$

$$S_0^+ = \frac{S_2S_1 + \overline{S_2}S_0 = S_2S_1 + \overline{S_2}\overline{S_1}}{\quad}$$

Problem 3 (19 points): Combinational logic structures

Consider the Boolean function $F(a,b,c) = \text{OR}(m_1, m_3, m_6, m_7)$, where m_i is minterm i .

 
1. (4 points) Let $G(a,b,c)$ be equal to $F(a,b,c)$, **except that input $abc=101$ will never arise.** Give a **minimal 2-level NAND gate** implementation of G . *Complemented inputs are available.*




2. (15 points) For each of the following circuits, does it implement $F(a,b,c) = \text{OR}(m_1, m_3, m_6, m_7)$? For each circuit, circle 'Yes' or 'No'.

Note: There is a *guessing penalty*: +3 for correct, 0 for blank, -2 for wrong.


(a) Yes No

 


(b) Yes No

 


(c) Yes No

 

(d) Yes No

 

(e) Yes No

 

Problem 4 (15 points): The LC-3 microprocessor

1. (3 points) List the state numbers that implement the entire instruction cycle of the LC-3 *STI* instruction.

Answer: 18, 33, 35, 32, 11, 29, 31, 23, 16

2. (12 points) Complete the following table by entering values (0, 1, or X) for the LC-3 microinstructions at ROM addresses 4 and 7.

Note: If the answer is 'don't care' then you **must use 'X'**.

ROM Address	IRD	COND(3)	J(6)	LD.BEN	LD.MAR	LD.MDR	LD.IR	LD.PC	LD.REG	LD.CC	GateMARMUX	GateMDR	GateALU	GatePC	MARMUX	PCMUX(2)	ADDR1MUX	ADDR2MUX(2)	DRMUX(2)	SR1MUX(2)	ALUK(2)	MIO.EN	R.W
4	0	011	010100	0	0	0	0	0	1	0	0	0	0	1	x	xx	x	xx	01	xx	xx	0	x
7	0	000	010111	0	1	0	0	0	0	0	1	0	0	0	1	xx	1	01	xx	01	xx	0	x

Problem 5 (22 points): The LC-3 microprocessor

In this problem we introduce a new instruction to the LC-3 instruction set, called **ANDMI**: AND from Memory with Immediate data.

ANDMI DR, SR, imm5

ANDMI has opcode 1101. It computes the bitwise AND of $\text{sext}(\text{imm5})$ and the memory word whose address is in register SR, and puts the result in the DR. **ANDMI** then sets the condition codes. The RTL is:

DR \leftarrow M[R(IR[8:6])] AND sext(imm5), Setcc

1. (4 points) Give the binary encoding of the instruction **ANDMI R3, R4, #-15**

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
1	1	0	1	0	1	1	1	0	0	1	1	0	0	0	1

2. (2 points) Why would **IR[5]=0** in the **ANDMI** instruction not work?

Answer: IR[5] must be 1 in order that the sext(imm5) operand is selected by the SR2MUX.

3. (8 points) In RTL form, give the sequence of 4 **microinstructions** that implement the **ANDMI** instruction **after the decode state**. If needed, you may use register R6 as a temporary register.

Answer: MAR \leftarrow R(IR[8:6])
MDR \leftarrow M[MAR]
R6 \leftarrow MDR
DR \leftarrow R6 AND sext(imm5), setCC


4. (2 points) The execute phase of **ANDMI** starts at what control ROM address?

Answer: 001101 (Answer in **binary** with the **correct number of bits**)

Problem 5 (continued)

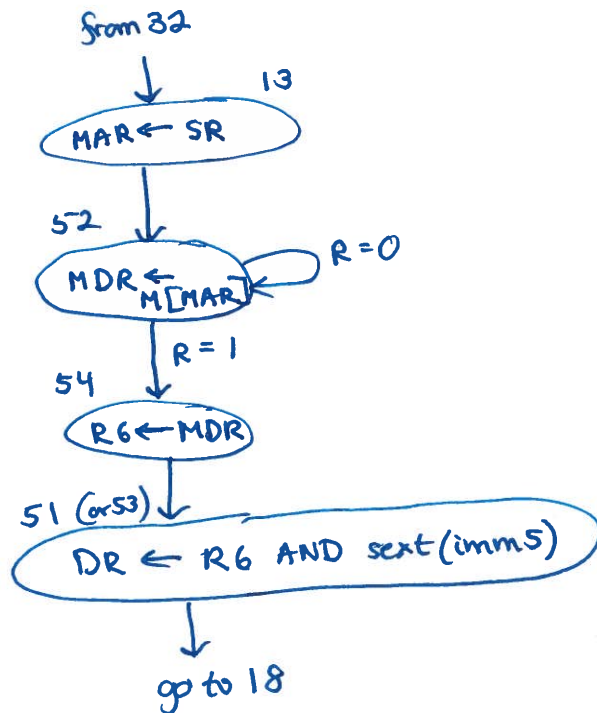5. (6 points) Draw the state diagram for **ANDMI**, including the state numbers after the decode state. When you need *additional* states, state numbers 51, 52, 53, and 54 are available for your use.

Note: $51_{10} = 110011_2$, $52_{10} = 110100_2$, $53_{10} = 110101_2$, $54_{10} = 110110_2$.




Problem 6 (20 points): LC-3 Assembly Program Analysis

1. (10 points) The following LC-3 program implements a guessing game. Complete the flowchart on the right for the same program.

```

OUTER    .ORIG      x3000
         LEA        R0, GUESS
         PUTS
INNER    LEA        R1, SECRET
         LDR        R2, R1, #0
         BRz       DONE
         ADD        R1, R1, #1
         GETC
         OUT
         NOT        R0, R0
         ADD        R0, R0, #1
         ADD        R0, R0, R2
         BRz       INNER
         LD         R0, NEWLINE
         OUT
         BRnzp    OUTER
DONE     HALT
NEWLINE .FILL      x0A
SECRET  .STRINGZ   "BYTE"
GUESS   .STRINGZ   "Guess: "
         .END

```

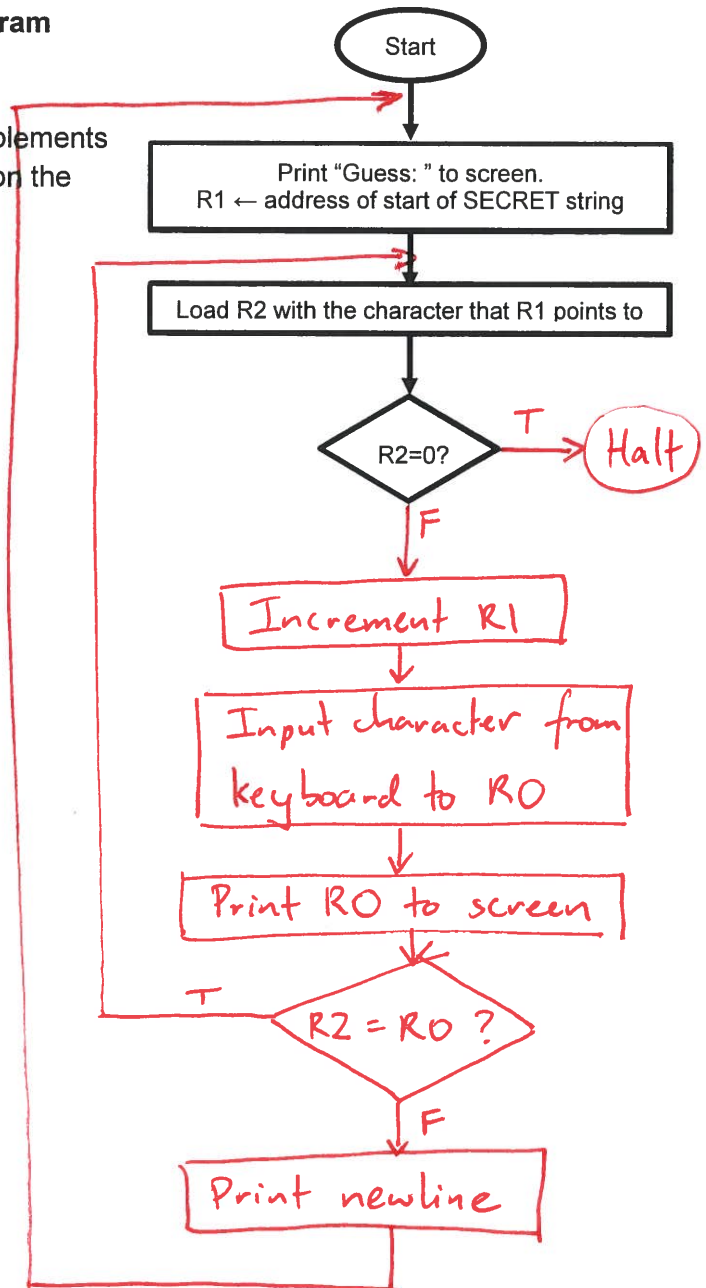

2. (10 points) Write down exactly what this program prints to screen when the user runs the program and enters **BITBYTE** using a keyboard. Note that GETC inputs a character from the keyboard but does not print anything to the screen.

Guess: BI

Guess: T

Guess: BYTE

Problem 7 (22 points): LC-3 Machine Code Debugging

1. (2 points) Define the Hamming weight of a value to be the number of 1s in its binary representation.

Write down the Hamming weight of the 16-bit value xECEB as a decimal number: _____

2. (20 points) The snippet of LC-3 machine code shown below is intended to compute the Hamming weight of a 16-bit value that is already provided in R1. The register usage is described now.

R1: initially contains the 16-bit value


R2: is used as a loop variable

R3: will contain the result (Hamming weight of the initial value in R1)

Unfortunately, there is exactly 1 bit in error in each LC-3 machine code instruction. First translate the original machine code exactly into original assembly code (leaving the errors in). Then debug the machine code by circling the bit error in each line and writing down the corrected assembly code. The first three lines and the last line have been completed for you.

Original Machine Code	Original Assembly Code	Corrected Assembly Code
0001 010 010 1 00000	ADD R2, R2, #0	AND R2, R2, #0
0001 010 010 1 01111	ADD R2, R2, #-1	ADD R2, R2, #15
0101 011 011 1 00000	AND R7, R3, #0	AND R3, R3, #0
0101 001 001 1 00000	AND R1, R1, #0	ADD R1, R1, #0
0000 011 00000000	BRzp #0	BRzp #1
0001 011 010 1 00001	ADD R3, R2, #1	ADD R3, R3, #1
0001 001 001 1 00001	ADD R1, R1, #1	ADD R1, R1, R1
0001 010 010 1 11101	ADD R2, R2, #-3	ADD R2, R2, #-1
0000 011 111111010	BRnzp #-6	BRzp #-6

LC-3 Control Word Fields

 


LC-3 Microsequencer Control

Signal	Description
--------	-------------

IRD $\begin{cases} = 1, \text{CAR} \leftarrow 000 \text{opcode (opcode} = \text{IR[15:12])}, \text{only during decode} \\ = 0, \text{CAR} \leftarrow \text{J (plus 1, 2, 4, 8, 16 depending on COND bits)} \end{cases}$

COND $\begin{cases} = 000, \text{CAR} \leftarrow \text{J} \\ = 001, \text{IF (R=1 and J[1]=0)} \text{ THEN (CAR} \leftarrow \text{J plus 2) ELSE (CAR} \leftarrow \text{J)} \\ = 010, \text{IF (BEN=1 and J[2]=0)} \text{ THEN (CAR} \leftarrow \text{J plus 4) ELSE (CAR} \leftarrow \text{J)} \\ = 011, \text{IF (IR[11]=1 and J[0]=0)} \text{ THEN (CAR} \leftarrow \text{J plus 1) ELSE (CAR} \leftarrow \text{J)} \end{cases}$

 J 6-bit next value for CAR (plus modifications depending on COND bits)



Fundamental Laws of Boolean Algebra

- Commutativity: $x \cdot y = y \cdot x$
- Associativity: $(x \cdot y) \cdot z = x \cdot (y \cdot z)$
- Distributivity: $x \cdot (y + z) = xy + xz$
- Idempotence: $x \cdot x = x$
- Identity: $x \cdot 1 = x$
- Null: $x \cdot 0 = 0$
- Complementarity: $x \cdot x' = 0$
- Involution: $(x')' = x$
- DeMorgan's: $(x \cdot y)' = x' + y'$
- Absorption: $x \cdot (x + y) = x$
- No-Name: $x \cdot (x' + y) = x \cdot y$
- Consensus: $(x+y) \cdot (y+z) \cdot (x'+z) = (x+y) \cdot (x'+z)$

IEEE 754 32-bit floating point format




The actual number represented in this format is:

$$(-1)^s \times 1.\text{mantissa} \times 2^{\text{exp.} - 127}$$

where $1 \leq \text{exponent} \leq 254$ for normalized representation.

LC-3 FSM

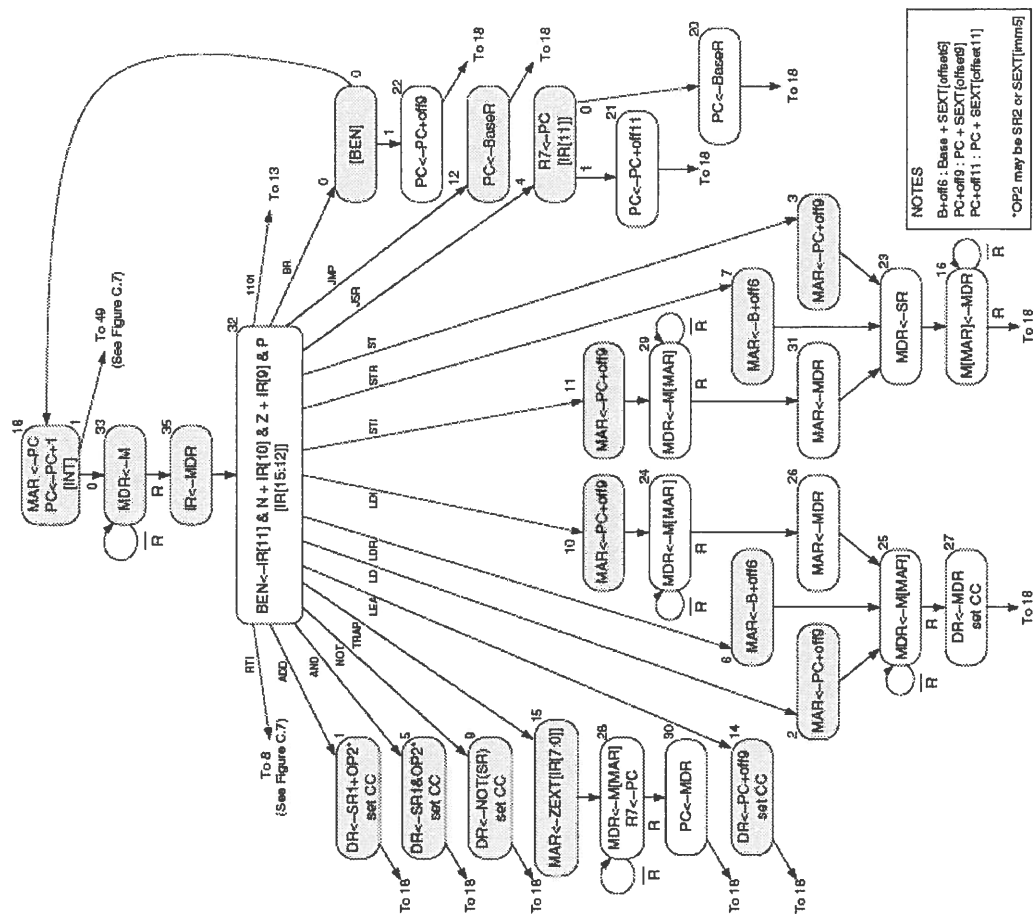

NOTES: RTL corresponds to execution (after fetch!); JSRR not shown

LC-3 Instructions

ADD	0001	DR	SR1	0	00	SR2	ADD DR, SR1, SR2	LD	0010	DR	PCoffset9	LD DR, PCoffset9	
							$DR \leftarrow SR1 + SR2, Setcc$					$DR \leftarrow M[PC + SEXT(PCoffset9)], Setcc$	
ADD	0001	DR	SR1	1	imm5		ADD DR, SR1, imm5	LDI	1010	DR	PCoffset9	LDI DR, PCoffset9	
							$DR \leftarrow SR1 + SEXT(imm5), Setcc$					$DR \leftarrow M[M[PC + SEXT(PCoffset9)]], Setcc$	
AND	0101	DR	SR1	0	00	SR2	AND DR, SR1, SR2	LDR	0110	DR	BaseR	offset6	LDR DR, BaseR, offset6
							$DR \leftarrow SR1 \text{ AND } SR2, Setcc$						$DR \leftarrow M[BaseR + SEXT(offset6)], Setcc$
AND	0101	DR	SR1	1	imm5		AND DR, SR1, imm5	LEA	1110	DR	PCoffset9		LEA DR, PCoffset9
							$DR \leftarrow SR1 \text{ AND } SEXT(imm5), Setcc$						$DR \leftarrow PC + SEXT(PCoffset9), Setcc$
BR	0000	n	z	p	PCoffset9		BR{nzp} PCoffset9	NOT	1001	DR	SR	111111	NOT DR, SR
							$\{(n \text{ AND } N) \text{ OR } (z \text{ AND } Z) \text{ OR } (p \text{ AND } P)\}: PC \leftarrow PC + SEXT(PCoffset9)$						$DR \leftarrow \text{NOT } SR, Setcc$
JMP	1100	000	BaseR	000000			JMP BaseR	ST	0011	SR	PCoffset9		ST SR, PCoffset9
							$PC \leftarrow BaseR$						$M[PC + SEXT(PCoffset9)] \leftarrow SR$
JSR	0100	1	PCoffset11				JSR PCoffset11	STI	1011	SR	PCoffset9		STI SR, PCoffset9
							$R7 \leftarrow PC, PC \leftarrow PC + SEXT(PCoffset11)$						$M[M[PC + SEXT(PCoffset9)]] \leftarrow SR$
TRAP	1111	0000	trapvect8				TRAP trapvect8	STR	0111	SR	BaseR	offset6	STR SR, BaseR, offset6
							$R7 \leftarrow PC, PC \leftarrow M[ZEXT(trapvect8)]$						$M[BaseR + SEXT(offset6)] \leftarrow SR$

LC-3 Datapath Control Signals

Signal	Description	Signal	Description
LD.MAR	= 1, MAR is loaded	LD.CC	= 1, updates status bits from system bus
LD.MDR	= 1, MDR is loaded	GateMARMUX	= 1, MARMUX output is put onto system bus
LD.IR	= 1, IR is loaded	GateMDR	= 1, MDR contents are put onto system bus
LD.PC	= 1, PC is loaded	GateALU	= 1, ALU output is put onto system bus
LD.REG	= 1, register file is loaded	GatePC	= 1, PC contents are put onto system bus
LD.BEN	= 1, updates Branch Enable (BEN) bit		
MARMUX	{ = 0, chooses ZEXT IR[7:0] = 1, chooses address adder output	MIO.EN	{ = 1, Enables memory, chooses memory output for MDR input = 0, Disables memory, chooses system bus for MDR input
ADDR1MUX	{ = 0, chooses PC = 1, chooses reg file SR1 OUT	R.W	{ = 1, M[MAR]←MDR when MIO.EN = 1 = 0, MDR←M[MAR] when MIO.EN = 1
ADDR2MUX	{ = 00, chooses "0...00" = 01, chooses SEXT IR[5:0] = 10, chooses SEXT IR[8:0] = 11, chooses SEXT IR[10:0]	ALUK	{ = 00, ADD = 01, AND = 10, NOT A = 11, PASS A
PCMUX	{ = 00, chooses PC + 1 = 01, chooses system bus = 10, chooses address adder output	DRMUX	{ = 00, chooses IR[11:9] = 01, chooses "111" = 10, chooses "110"
SR1MUX	{ = 00, chooses IR[11:9] = 01, chooses IR[8:6] = 10, chooses "110"		

LC-3 Datapath

