

**ECE 198JL Second Midterm Exam  
Spring 2013**

Tuesday, March 5<sup>th</sup>, 2013

Name:	_____	NetID:	_____
Discussion Section:			
10:00 AM	<input type="checkbox"/>	JD1	_____
11:00 AM	<input type="checkbox"/>	JD2	_____
2:00 PM	<input type="checkbox"/>	JD3	_____
4:00 PM	<input type="checkbox"/>	JD4	_____

- **Be sure your exam booklet has 10 pages.**
- **Be sure to write your name and lab section on the first page.**
- **Do not tear the exam booklet apart; you can only detach the last page.**
- **We have provided Boolean properties at the back.**
- **Use backs of pages for scratch work if needed.**
- **This is a closed book exam. You may not use a calculator.**
- **You are allowed one handwritten 8.5 x 11" sheet of notes.**
- **Absolutely no interaction between students is allowed.**
- **Be sure to clearly indicate any assumptions that you make.**
- **The questions are not weighted equally. Budget your time accordingly.**
- **Don't panic, and good luck!**

Problem 1	11 points:	_____
Problem 2	14 points:	_____
Problem 3	15 points:	_____
Problem 4	10 points:	_____
Problem 5	22 points:	_____
Problem 6	18 points:	_____
Problem 7	10 points:	_____

---

Total	100 points:	_____
-------	-------------	-------

**Problem 1 (11 pts): Boolean algebra**

1. Simplify expression  $y'(x'z+y'z)'$ . Write each step separately in the space provided. Name the property used for each step. First step is already written for you. (Refer to Boolean algebra properties on the last page of the exam booklet.)

$y'(x'z+y'z)'$	Property
$= y'(x'z)'(y'z)'$	DeMorgan
$= y'(x+z')(y+z')$	DeMorgan
$= y'(xy+z')$	Distributivity
$= y'xy + y'z'$	Distributivity
$= xy y' + y'z'$	Commutativity
$= x \cdot 0 + y'z'$	Complementarity
$= 0 + y'z'$	Null
$= y'z'$	Identity

2. Prove by **perfect induction** consensus property:  $xy + yz + x'z = xy + x'z$

X	Y	Z	$xy + yz + x'z$	$xy + x'z$
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	1

Since the truth tables for both functions are the same, then they must be equivalent

3. Write dual for  $x+y'z x' + 0 \cdot x$ . **Do not simplify.**

Answer:  $x(y'z + x')(1+x)$

4. Let  $f(w, x, y, z) = m_9$ . Find its dual and write it in  $M_i$  notation.

Answer:  $M_6$

$m_9 = w x' y' z \rightarrow \text{Dual: } w + x' + y' + z = M_6$

**Problem 2 (14 pts): Canonical forms**

A committee has members A, B, and C. Variables a, b, c have value 1 iff A, B, C respectively vote in favor of a proposal. Design a combinational circuit whose output g is 1 iff there is a majority in favor.

1. Fill in truth table.

a	b	c	g
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

2. Using above table, write **canonical SOP** representation using **literals**.

Answer: 
$$g = a'bc + ab'c + abc' + abc$$

3. Using above table, write **canonical SOP** representation using **minterm** notation  $m_i$ .

Answer: 
$$g = m_3 + m_5 + m_6 + m_7$$

4. Using above table, write **canonical POS** representation using **literals**.

Answer: 
$$g = (a + b + c)(a + b + c')(a + b' + c)(a' + b + c)$$

5. Using above table, write **canonical POS** representation using **maxterm** notation  $M_i$ .

Answer: 
$$g = M_0 M_1 M_2 M_4$$

6. For function  $f(a, b, c, d) = a'bc + a'cd'$ , write corresponding **canonical SOP**.

Answer: 
$$f = a'bcd' + a'bcd + a'b'cd'$$

7. For function  $g(w, x, y, z) = (w+x')(w+x'+y+z')$ , write corresponding **canonical POS**.

Answer: 
$$g = (w+x'+y'+z')(w+x'+y+z')(w+x'+y+z')(w+x'+y+z)$$

**Problem 3 (15 pts): Function simplification**

Consider a 4-variable Boolean function  $f(w, x, y, z)$  given by its K-map (drawn twice):

		yz			
		00	01	11	10
wx	00	X	0	1	1
	01	1	0	1	X
	11	1	1	0	0
	10	0	X	0	1

		yz			
		00	01	11	10
wx	00	X	0	1	1
	01	1	0	1	X
	11	1	1	0	0
	10	0	X	0	1

1. List the **essential prime implicants**.

Answer:  $w'y$  and  $x'yz'$

2. Give a **minimal SOP** expression for  $f(w, x, y, z)$  and **show the corresponding loops on the left map**.

Answer:  $f = w'y + x'yz' + w'z' + wx y'$

3. Give a **minimal POS** expression for  $f(w, x, y, z)$  and **show the corresponding loops on the right map**.

Answer:  $f = (x+y)(w+y+z')(w'+y+z')(w'+x'+y')$   
 (The solution is not unique, other minimal POS exist)

4. Do your answers to **Part 2** and **Part 3** represent the same Boolean function? Justify your answer.

No, because their values for the "don't cares" may differ. For example:

Part 2:  $f(0,0,0,0) = 1$       Part 3:  $f(0,0,0,0) = 0$


5. Let  $g(x, y, z) = x(y \oplus z)$ . Fill in its K-map on the right and write **minimal POS** below. Show the corresponding loops.

Answer:  $g = x(y+z)(y'+z')$


		yz			
		00	01	11	10
x	0	0	0	0	0
	1	0	1	0	1
		$g(x, y, z)$			

**Problem 4 (10 pts): 2-level circuits**

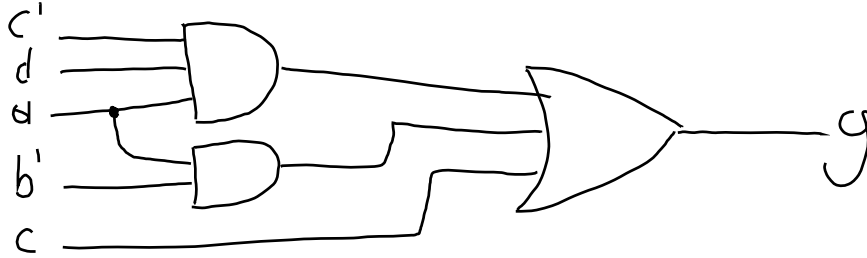1. Implement Boolean function  $g(a, b, c, d) = ac'd + ab' + c$  as a two-level network using **AND** and **OR** gates **only**. Assume that inverted inputs are available. Draw the circuit.



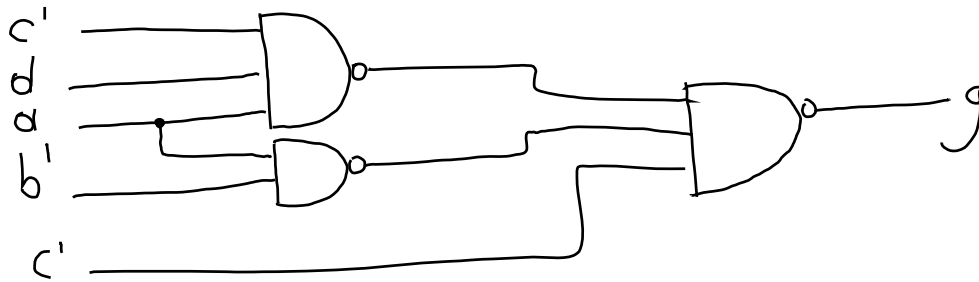2. Re-implement the same function using **NAND** gates **only**. Do not use more than 6 NAND gates. Assume that inverted inputs are available. Draw the circuit.




3. Re-implement the same function using a **4:1 MUX** and no more than **one extra gate**. Assume that inverted inputs are available. Draw the circuit. Show your work. *Hint: Draw K-map.*

Hand-drawn Karnaugh map for the function  $g(a, b, c, d) = ac'd + ab' + c$ . The vertical axis is labeled  $ab$  and the horizontal axis is labeled  $cd$ .

		$cd$			
		$00$	$01$	$11$	$10$
$00$		0	0	1	1
$01$		0	0	1	1
$11$		0	1	1	1
$10$		1	1	1	1


Hand-drawn truth table analysis for the MUX implementation:

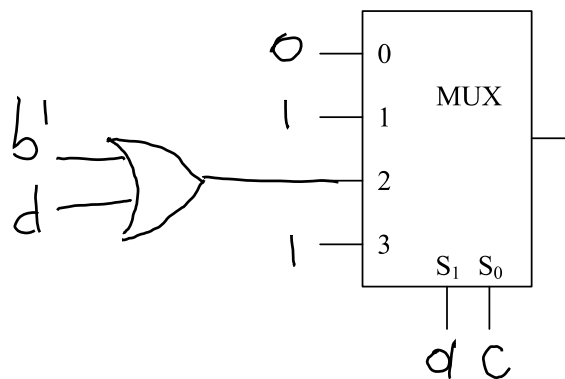- $a=0, c=0 \Rightarrow g=0$
- $a=0, c=1 \Rightarrow g=1$
- $a=1, c=0 \Rightarrow g=b' + d$
- $a=1, c=1 \Rightarrow g=1$



**Problem 5 (22 pts): Combinational logic design**

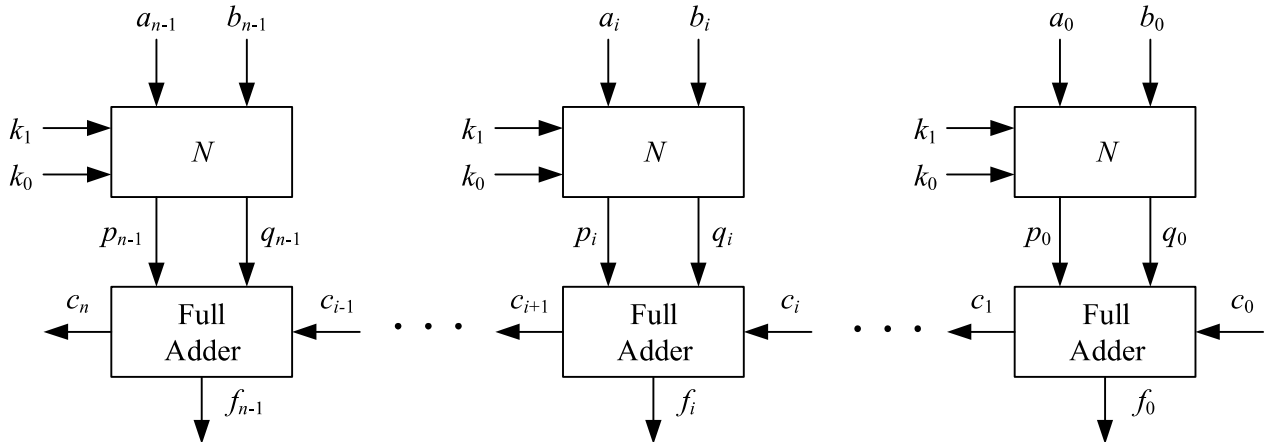**Part A.** An n-bit arithmetic unit takes inputs  $A=a_{n-1} \dots a_0$  and  $B=b_{n-1} \dots b_0$ , interpreted as the n-bit two's-complement representations of numbers.



The control signals are  $k_1, k_0$ , and  $c_0$  (the carry-in to stage 0). At each stage  $i$ , the inputs to the full adder are

$$p_i = a_i k_1' k_0 + b_i k_1$$

$$q_i = a_i k_1' k_0' + b_i k_1 + b_i' k_0$$

$k_1$	$k_0$	$p_i$	$q_i$
0	0	0	$a_i$
0	1	$a_i$	$b_i$
1	0	$b_i$	$b_i$
1	1	$b_i$	1

1. Determine the function of A and B produced by each of the following combinations of control signals:

2. Determine the values for the control signals to produce each of the following functions:

$k_1$	$k_0$	$c_0$	Function
0	1	1	$A - B$
1	0	0	$2B$

Function	$k_1$	$k_0$	$c_0$
A plus 1	0	0	1
B minus 1	1	1	0


*Hint:* write out truth tables for  $p_i$  and  $q_i$  as functions of  $k_1$  and  $k_0$ .

3. Write  $c_0$  as a function of  $k_1$  and  $k_0$ .

Answer:  $c_0 = k_1'$

$k_1, k_0$	$c_0$
0 0	1
0 1	1
1 0	0
1 1	0

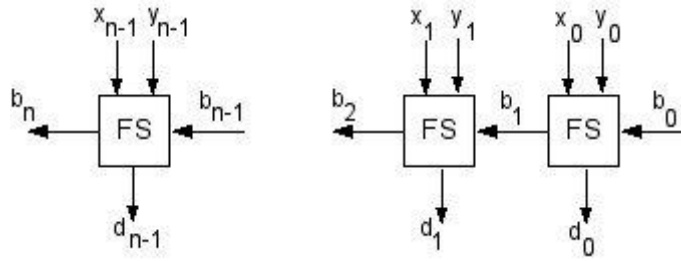**Part B.** You are designing a Full Subtractor (FS) circuit. The FS has inputs  $x_i, y_i$ , and a borrow input  $b_i$ . There are two outputs: difference  $d_i$  and borrow-out  $b_{i+1}$ .



The FS cell should be designed so that the n-bit subtractor network shown above correctly computes  $D=X-Y$ , where  $X = x_{n-1} \dots x_1x_0$  and  $Y = y_{n-1} \dots y_1y_0$  are nonnegative n-bit binary numbers. Assume  $X \geq Y$ .

Examples for n=3:

	X	$x_2x_1x_0$	101	100
-	Y	$y_2y_1y_0$	<u>011</u>	<u>001</u>
	D	$d_2d_1d_0$	010	011

1. Draw K-maps for  $d_i$  and for  $b_{i+1}$ . *Hint:* Remember that  $b_{i+1}$  and  $d_i$  are functions of only the 3 inputs:  $x_i, y_i, b_i$ . Try some examples, and start with the rightmost FS cell.

		$x_iy_i$			
		00	01	11	10
$b_i$	0	0	1	0	1
	1	1	0	1	0
		$d_i$			

		$x_iy_i$			
		00	01	11	10
$b_i$	0	0	1	0	0
	1	1	1	1	0
		$b_{i+1}$			

$$d_i = (b_i + x_i + y_i)(b_i' + x_i + y_i')(b_i + x_i' + y_i')(b_i' + x_i' + y_i') \quad (\text{POS})$$


2. Give minimal POS expressions for  $d_i$  and for  $b_{i+1}$ .

$$d_i = \underline{b_i x_i' y_i' + b_i' x_i y_i + b_i x_i y_i + b_i' x_i' y_i} \quad (\text{SOP})$$

$$b_{i+1} = \underline{(b_i + y_i)(b_i + x_i')(x_i' + y_i)}$$

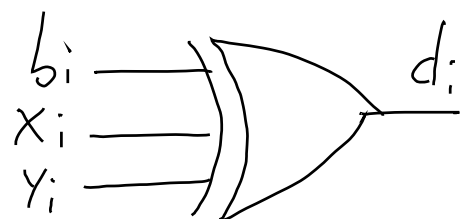
3. Implement circuit for computing  $d_i$  value using XOR gate(s) only.

$$\begin{aligned} d_i &= b_i' (x_i \oplus y_i) + b_i (x_i' y_i' + x_i y_i) \\ &= b_i' (x_i \oplus y_i) + b_i (\overline{x_i \oplus y_i}) \\ &= b_i \oplus x_i \oplus y_i \end{aligned}$$



**Problem 6 (18 pts): Sequential logic components**

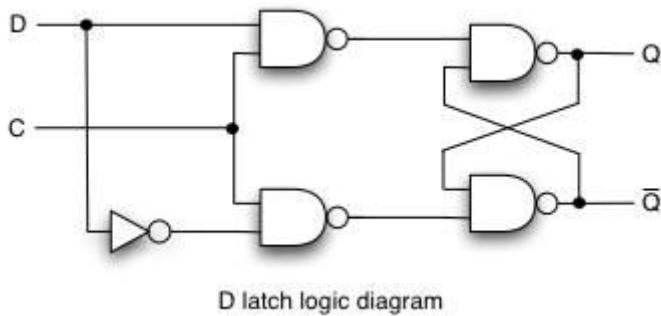**Part A.** Shown below is the logic diagram of a gated D latch. It consists of 4 NAND gates and an inverter. It has 2 inputs: D and C.



1. Complete the next-state table for this latch circuit.


C	D	Q+
0	0	Q
0	1	Q
1	0	0
1	1	1

2. Express next state Q+ as a function of C, D, and Q.

Answer:  $Q^+ = QC' + DC$

**Part B.** Complete the design of a 3-bit register that performs the operations listed in the table to the right. Parallel load inputs are labeled and indexed as  $P_i$ . Serial input is labeled as  $S_{in}$ . You may use inputs without drawing the wires, just write the appropriate labels at the ~~MUX~~ inputs.

$F_1$	$F_0$	Operation
0	0	Parallel load
0	1	Circular shift right
1	0	Logical shift left
1	1	No change

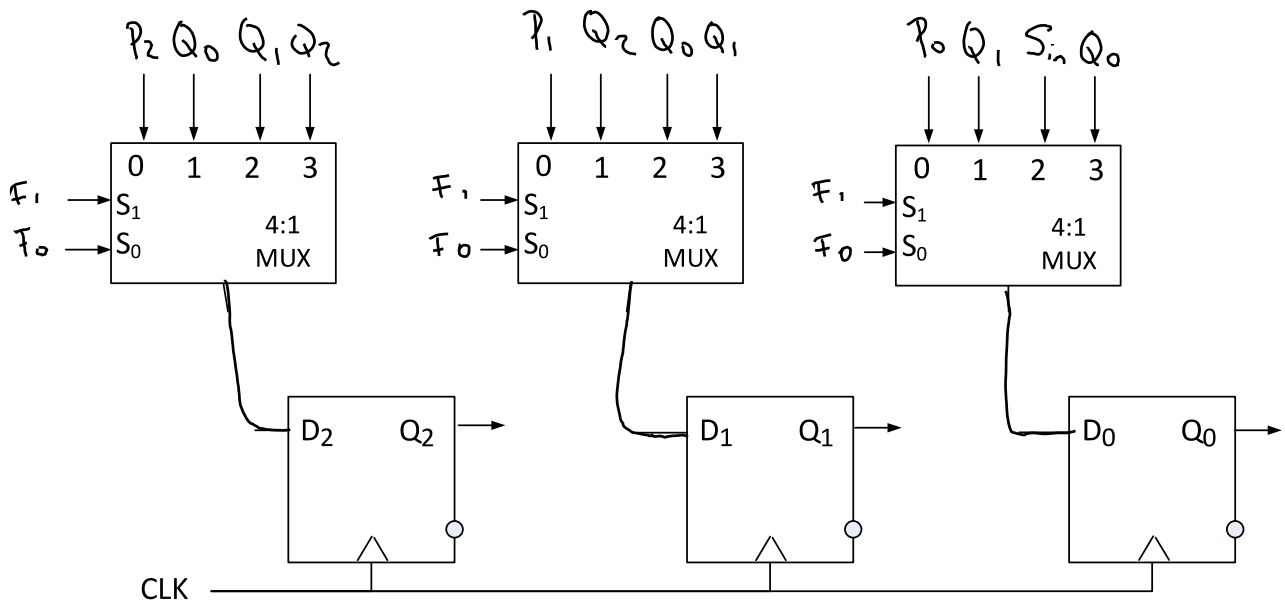



**Problem 7 (10 pts): Program analysis**

Consider the following C program:

```

#include <stdio.h>

int main()
{
    unsigned int a,b,c;
    int function;
    int notfirst=0;

    for ( a = 0; a <= 1; a = a + 1 )
    {
        for ( b = 0; b <= 1; b = b + 1 )
        {
            for ( c = 0; c <= 1; c = c + 1 )
            {
                function = a & (b | ~c);  $f = a(b+c')$ 
                if (function)
                {
                    if (notfirst) printf("+");
                    if (a) printf("a"); else printf("a'");
                    if (b) printf("b"); else printf("b'");
                    if (c) printf("c"); else printf("c'");
                    notfirst = 1;
                }
            }
        }
    }

    printf("\n");

    return 0;
}

```

Prints  
minterms  
of function

1. Write down EXACTLY the formatted text that will be printed on the terminal screen by the program.

$a'b'c' + ab'c' + abc$

2. Explain in one sentence the function of the program; that is, what does it print?

It prints the canonical SOP of the boolean function  $f = a(b+c')$

**Boolean algebra properties**

Commutativity	$x \cdot y = y \cdot x$	$x + y = y + x$
Associativity	$(x \cdot y) \cdot z = x \cdot (y \cdot z)$	$(x + y) + z = x + (y + z)$
Distributivity	$x \cdot (y + z) = x \cdot y + x \cdot z$	$x + y \cdot z = (x + y) \cdot (x + z)$
Idempotence	$x \cdot x = x$	$x + x = x$
Identity	$x \cdot 1 = x$	$x + 0 = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$
Complementarity	$x \cdot x' = 0$	$x + x' = 1$
Involution		$(x')' = x$
DeMorgan's	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$
Absorption	$x \cdot (x + y) = x$	$x + x \cdot y = x$
No-Name	$x \cdot (x' + y) = x \cdot y$	$x + x' \cdot y = x + y$
Consensus	$(x+y) \cdot (y+z) \cdot (x'+z) =$ $(x+y) \cdot (x'+z)$	$x \cdot y + y \cdot z + x' \cdot z =$ $x \cdot y + x' \cdot z$