

**ECE 120 Second Midterm Exam
Spring 2016**

Tuesday, March 15, 2016

Name: _____	NetID: _____
Discussion Section:	
9:00 AM	<input type="checkbox"/> AB1
10:00 AM	<input type="checkbox"/> AB2
11:00 AM	<input type="checkbox"/> AB3
12:00 PM	<input type="checkbox"/> AB4
1:00 PM	<input type="checkbox"/> AB5 <input type="checkbox"/> ABA
2:00 PM	<input type="checkbox"/> AB6
3:00 PM	<input type="checkbox"/> AB7 <input type="checkbox"/> ABB
4:00 PM	<input type="checkbox"/> AB8 <input type="checkbox"/> ABC
5:00 PM	<input type="checkbox"/> AB9 <input type="checkbox"/> ABD

- **Be sure that your exam booklet has 8 pages.**
- **Write your name, netid and check discussion section on the title page.**
- **Do not tear the exam booklet apart.**
- **Use backs of pages for scratch work if needed.**
- **This is a closed book exam. You may not use a calculator.**
- **You are allowed one handwritten 8.5 x 11" sheet of notes (both sides).**
- **Absolutely no interaction between students is allowed.**
- **Clearly indicate any assumptions that you make.**
- **The questions are not weighted equally. Budget your time accordingly.**
- **Show your work.**

Problem 1 20 points _____

Problem 2 19 points _____

Problem 3 18 points _____

Problem 4 14 points _____


Problem 5 17 points _____

Problem 6 12 points _____

Total 100 points _____

Problem 1 (20 points): CMOS and Boolean properties

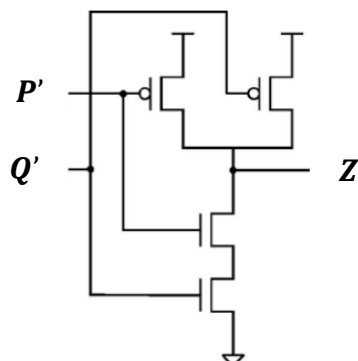1. (5 points) Circle the correct choice for each statement. **The inputs are inverted.**



a. The output Z equals:

P AND Q P OR Q P NOR Q P XOR Q P XNOR Q

b. This example best illustrates the Boolean property:

DeMorgan's Absorption No-Name Consensus

2. (15 points) Let $G(x,y,z)$ and $H(x,y,z)$ be the 3-variable functions whose K-maps are given below.

$G(x,y,z)$

		yz			
		00	01	11	10
x	0	0	1	1	0
	1	0	1	0	0

$H(x,y,z)$

		yz			
		00	01	11	10
x	0	0	1	1	1
	1	1	1	1	0

a. Express $H(x,y,z)$ in **canonical POS form**

i. Using the **variables** x, y, z :

$H(x,y,z) =$ _____

ii. Using the **maxterm M_i notation**:

$H(x,y,z) =$ _____

b. Using your expression for H from part a.i), give the exact **dual of H**:

dual of $H(x,y,z) =$ _____


c. Complete the K-map (below) for function F , so that $F + G = H$. **You must use don't cares wherever possible.**

$F(x,y,z)$

		yz			
		00	01	11	10
x	0				
	1				

Problem 2 (19 points): Sequential logic

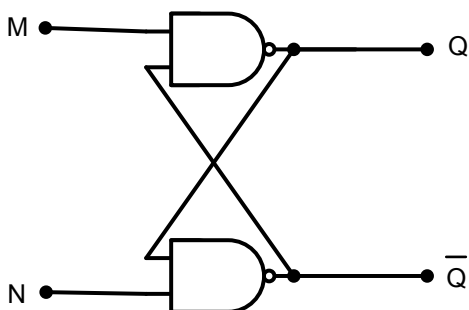1. (10 points) Consider the sequential feedback circuit shown below.




a. Complete the next-state table for this circuit

M	N	Q^+
0	0	Forbidden
0	1	
1	0	
1	1	

b. Express the next state Q^+ as a function of M , N , and Q in **SOP form**.

$Q^+ =$ _____

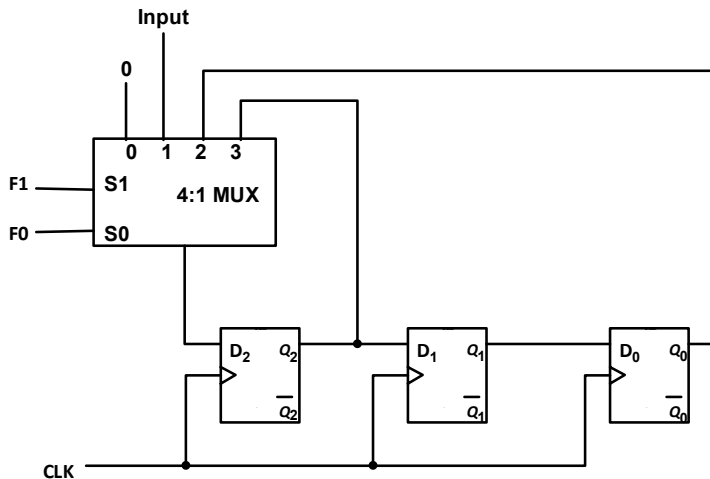2. (9 points) Consider a 3-bit shift register that has the following diagram:



a. Determine the functionality of the register by completing the following table

F_1	F_0	Operation
0	0	Unused
0	1	
1	0	
1	1	

b. If the shift register initially stores $Q_2Q_1Q_0=100$ and $Input=0$, what is stored in the register after one clock pulse and

$F_1 F_0 = 01$? _____

$F_1 F_0 = 10$? _____ (Assume again that 100 is stored before the operation.)

$F_1 F_0 = 11$? _____ (Assume again that 100 is stored before the operation.)

Problem 3 (18 points)

Consider the 4-variable function $f(w,x,y,z)$, with the following K-map (drawn twice).

		yz			
		00	01	11	10
wx	00	1	x	0	1
	01	0	1	1	0
	11	0	0	1	x
	10	1	1	0	1

minimal SOP
 $f(w,x,y,z)$

		yz			
		00	01	11	10
wx	00	1	x	0	1
	01	0	1	1	0
	11	0	0	1	x
	10	1	1	0	1

minimal POS
 $f(w,x,y,z)$


1. Give a **minimal SOP** expression for $f(w,x,y,z)$ and show the corresponding loops on the **left map**.

min SOP: _____

2. Give a **minimal POS** expression for $f(w,x,y,z)$ and show the corresponding loops on the **right map**.


min POS: _____

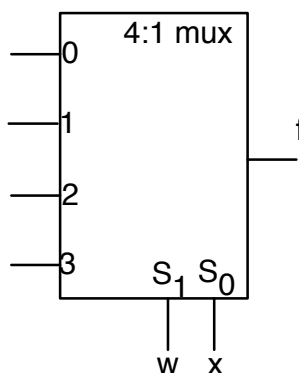3. Implement f using **only a 4:1 multiplexer** (with select inputs $S_1S_0 = wx$) and **one NAND gate**. Complemented inputs are **not** available.



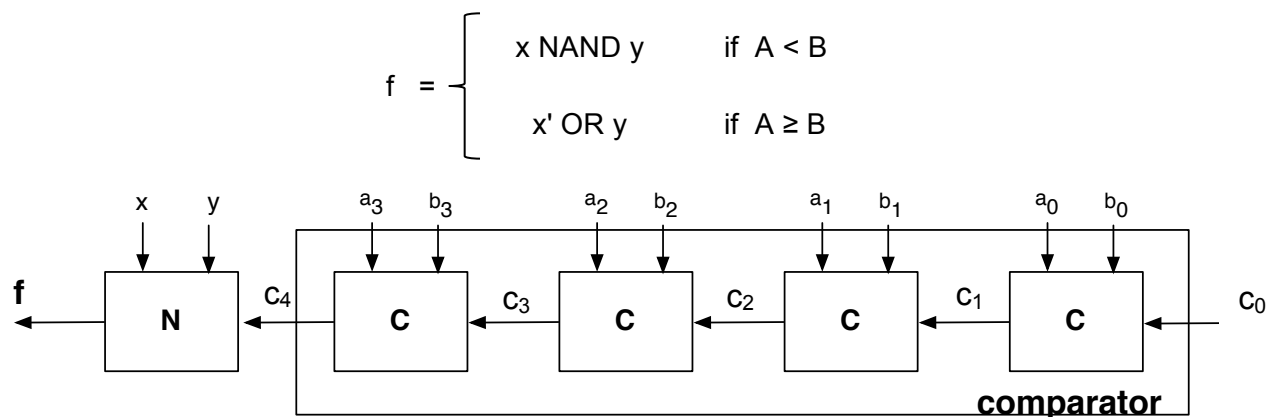Problem 4 (14 points)

In this problem you will complete the design of the circuit shown below, which compares two 4-bit unsigned binary numbers $A=a_3a_2a_1a_0$ and $B=b_3b_2b_1b_0$ and outputs



1. (8 points) Design cell C so that the comparator portion of the above circuit operates correctly and outputs

$$C_4 = \begin{cases} 0 & \text{if } A < B \\ 1 & \text{if } A \geq B \end{cases}$$

- a. Specify the input c_0 .

$c_0 =$ _____

- b. Express c_{i+1} in terms of c_i, a_i, b_i .

$c_{i+1} =$ _____

2. (6 points) Design the network N by giving a Boolean expression for f .


$f =$ _____

Problem 5 (17 points)

Shown below is an **8-bit arithmetic unit (AU)** which operates on two 8-bit **2's complement** numbers A and B. Each network N computes a^* and b^* , where:

$$a^* = k_1' k_0' + k_1 a$$
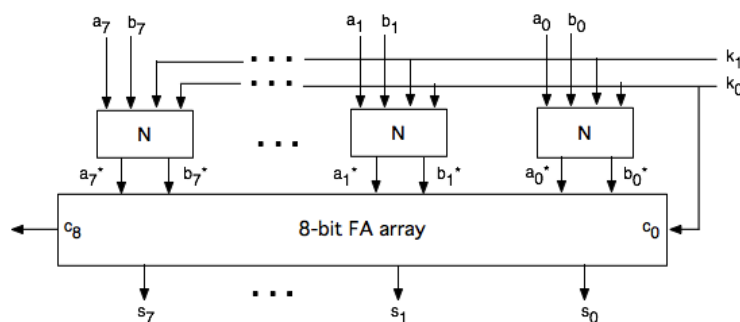
$$b^* = k_1 k_0' b' + k_0 b + k_1' k_0' a$$




- (4 points) Give a **2-level NAND gate** implementation of a^* . Assume complemented inputs are available.

- (13 points) Complete the table below.
 - Give the values for a^* , b^* , c_0
 - Specify the operation performed. Express your answer as an **arithmetic function (PLUS/MINUS)** of **A and B** (e.g., “a plus the complement of b” is not an appropriate response).

k_1	k_0	a^*	b^*	c_0	Operation performed as a function of A and B (e.g. A PLUS/MINUS B)
0	0				
0	1				
1	0				
1	1				

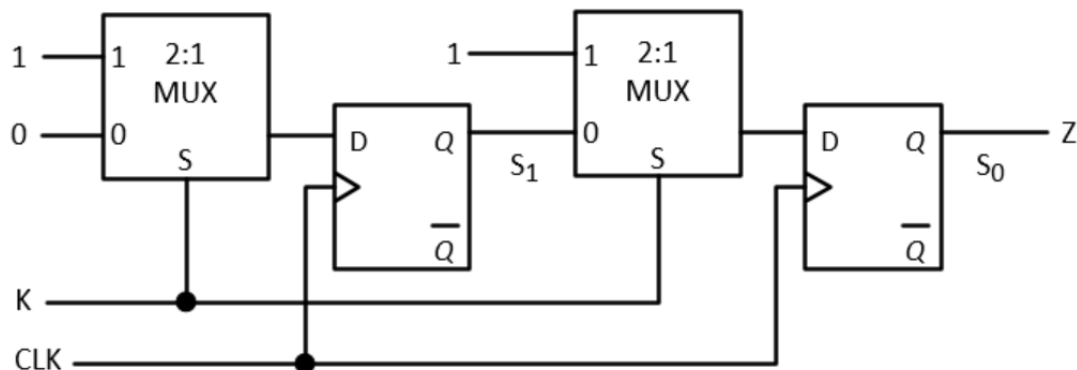Problem 6 (12 points): Finite State Machines






The circuit below is a 2-bit register that shifts right with serial input of 0 when $K=0$ and parallel loads with inputs of 1 when $K=1$.



1. (6 points) Complete the state transition table for the circuit.

S_1	S_0	K	S_1^+	S_0^+	Z
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

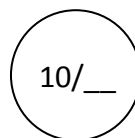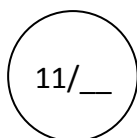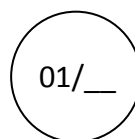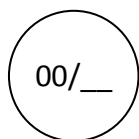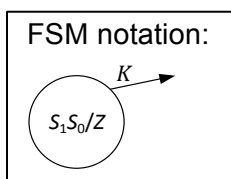2. (6 points) Complete the state transition diagram for the circuit.



Boolean algebra properties

Commutativity	$x \cdot y = y \cdot x$	$x + y = y + x$
Associativity	$(x \cdot y) \cdot z = x \cdot (y \cdot z)$	$(x + y) + z = x + (y + z)$
Distributivity	$x \cdot (y + z) = x \cdot y + x \cdot z$	$x + y \cdot z = (x + y) \cdot (x + z)$
Idempotence	$x \cdot x = x$	$x + x = x$
Identity	$x \cdot 1 = x$	$x + 0 = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$
Complementarity	$x \cdot x' = 0$	$x + x' = 1$
Involution		$(x')' = x$
DeMorgan's	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$
Absorption	$x \cdot (x + y) = x$	$x + x \cdot y = x$
No-Name	$x \cdot (x' + y) = x \cdot y$	$x + x' \cdot y = x + y$
Consensus	$(x+y) \cdot (y+z) \cdot (x'+z) =$ $(x+y) \cdot (x'+z)$	$x \cdot y + y \cdot z + x' \cdot z =$ $x \cdot y + x' \cdot z$

Feel free to tear this page off and use it as scratch paper.