

**ECE 120 Second Midterm Exam
Spring 2016**

Tuesday, March 15, 2016

Name: _____	NetID: _____	
SOLUTIONS		
Discussion Section:		
9:00 AM	<input type="checkbox"/> AB1	
10:00 AM	<input type="checkbox"/> AB2	
11:00 AM	<input type="checkbox"/> AB3	
12:00 PM	<input type="checkbox"/> AB4	
1:00 PM	<input type="checkbox"/> AB5	<input type="checkbox"/> ABA
2:00 PM	<input type="checkbox"/> AB6	
3:00 PM	<input type="checkbox"/> AB7	<input type="checkbox"/> ABB
4:00 PM	<input type="checkbox"/> AB8	<input type="checkbox"/> ABC
5:00 PM	<input type="checkbox"/> AB9	<input type="checkbox"/> ABD


- Be sure that your exam booklet has 8 pages.
- Write your name, netid and check discussion section on the title page.
- Do not tear the exam booklet apart.
- Use backs of pages for scratch work if needed.
- This is a closed book exam. You may not use a calculator.
- You are allowed one handwritten 8.5 x 11" sheet of notes (both sides).
- Absolutely no interaction between students is allowed.
- Clearly indicate any assumptions that you make.
- The questions are not weighted equally. Budget your time accordingly.
- Show your work.

Problem 1	20 points	_____
Problem 2	19 points	_____
Problem 3	18 points	_____
Problem 4	14 points	_____
Problem 5	17 points	_____
Problem 6	12 points	_____

Total	100 points	_____
-------	------------	-------

Problem 1 (20 points): CMOS and Boolean properties

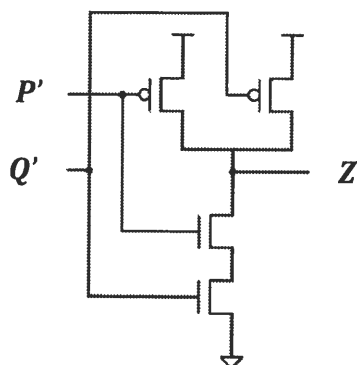1. (5 points) Circle the correct choice for each statement. **The inputs are inverted.**



a. The output Z equals:

P AND Q **P OR Q** P NOR Q P XOR Q P XNOR Q

b. This example best illustrates the Boolean property:

DeMorgan's Absorption No-Name Consensus

2. (15 points) Let $G(x,y,z)$ and $H(x,y,z)$ be the 3-variable functions whose K-maps are given below.

$G(x,y,z)$

		yz			
		00	01	11	10
x	0	0	1	1	0
	1	0	1	0	0

$H(x,y,z)$

		yz			
		00	01	11	10
x	0	0	1	1	1
	1	1	1	1	0

a. Express $H(x,y,z)$ in **canonical POS form**

i. Using the **variables** x, y, z :

$H(x,y,z) = \underline{(x+y+z)(x'+y'+z)}$

ii. Using the **maxterm M_i** notation:

$H(x,y,z) = \underline{M_0 M_6}$

b. Using your expression for H from part a.i), give the exact **dual of H** :

dual of $H(x,y,z) = \underline{xyz + x'y'z}$


c. Complete the K-map (below) for function F , so that $F \oplus G = H$. You must use don't cares wherever possible.

$F(x,y,z)$

		yz			
		00	01	11	10
x	0	0	x	x	1
	1	1	x	1	0

Problem 2 (19 points): Sequential logic

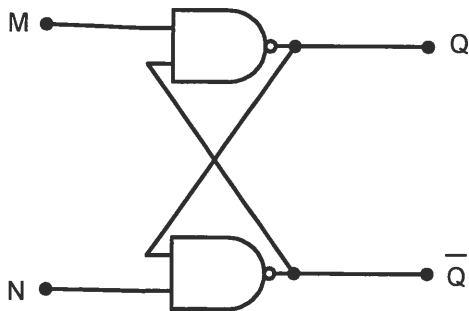1. (10 points) Consider the sequential feedback circuit shown below.



a. Complete the next-state table for this circuit


M	N	Q ⁺
0	0	Forbidden
0	1	1
1	0	0
1	1	Q

b. Express the next state Q⁺ as a function of M, N, and Q in SOP form.

$$Q^+ = M'N + MNQ = M' + MNQ = M'NQ' + M'NQ + MNQ$$

$$= M'N + NQ = M' + NQ$$

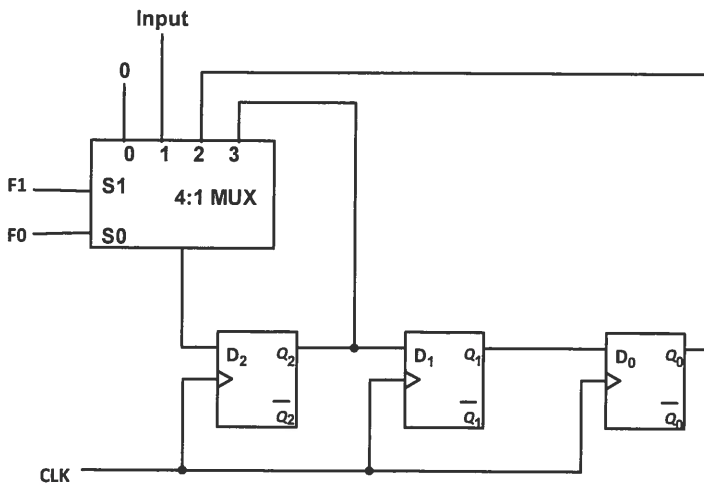2. (9 points) Consider a 3-bit shift register that has the following diagram:



a. Determine the functionality of the register by completing the following table

F ₁	F ₀	Operation
0	0	Unused
0	1	logical shift right
1	0	Circular shift right
1	1	Arithmetic shift right

b. If the shift register initially stores Q₂Q₁Q₀=100 and Input=0, what is stored in the register after one clock pulse and


F₁ F₀ = 01? 010

F₁ F₀ = 10? 010 (Assume again that 100 is stored before the operation.)

F₁ F₀ = 11? 110 (Assume again that 100 is stored before the operation.)

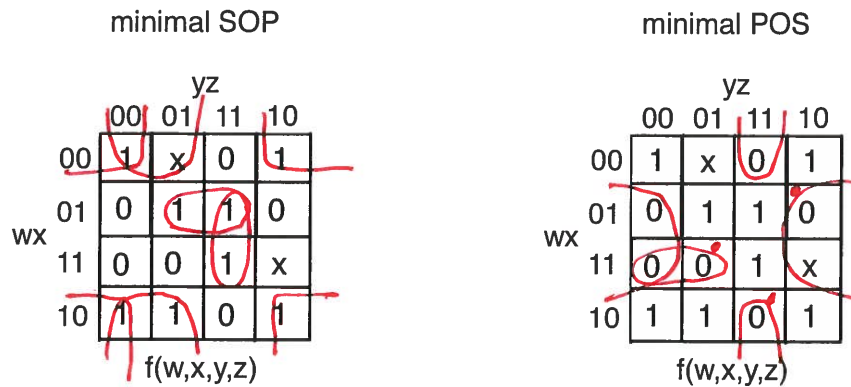Problem 3 (18 points)

Consider the 4-variable function $f(w,x,y,z)$, with the following K-map (drawn twice).




1. Give a **minimal SOP** expression for $f(w,x,y,z)$ and show the corresponding loops on the left map.

min SOP: $\bar{x}\bar{z} + \bar{x}\bar{y} + \left. \begin{matrix} \bar{w}\bar{y}z + xyz \\ \bar{w}xz + xyz \\ \bar{w}xz + wxy \end{matrix} \right\}$

2. Give a **minimal POS** expression for $f(w,x,y,z)$ and show the corresponding loops on the right map.


min POS: $(\bar{x} + z)(\bar{w} + \bar{x} + y)(x + \bar{y} + \bar{z})$

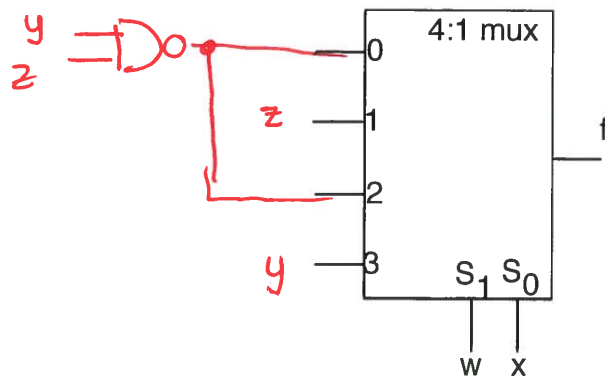3. Implement f using **only a 4:1 multiplexer** (with select inputs $S_1S_0 = wx$) and **one NAND gate**. Complemented inputs are **not** available.



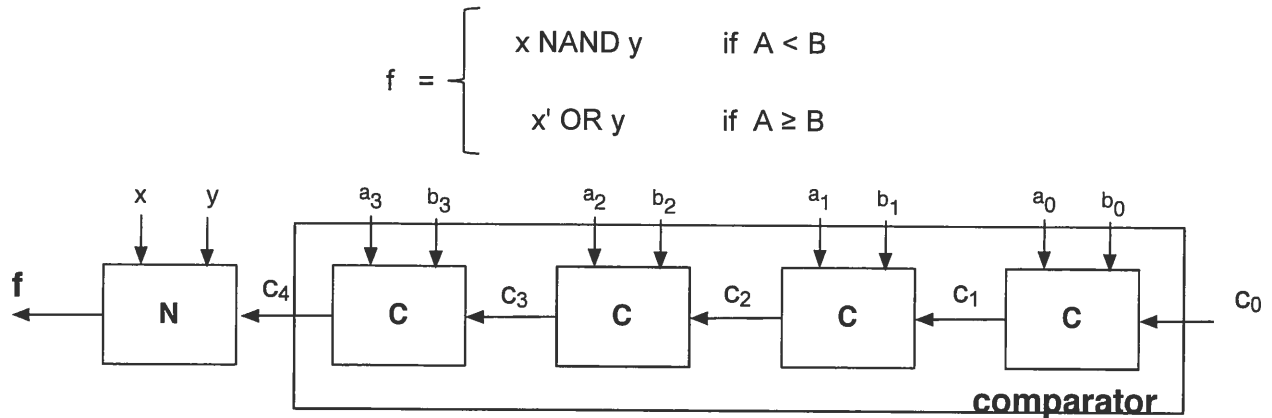Problem 4 (14 points)

In this problem you will complete the design of the circuit shown below, which compares two 4-bit unsigned binary numbers $A=a_3a_2a_1a_0$ and $B=b_3b_2b_1b_0$ and outputs



1. (8 points) Design cell C so that the comparator portion of the above circuit operates correctly and outputs

$$c_4 = \begin{cases} 0 & \text{if } A < B \\ 1 & \text{if } A \geq B \end{cases}$$

- a. Specify the input c_0 .

$c_0 =$ 1

- b. Express c_{i+1} in terms of c_i , a_i , b_i .

$c_{i+1} =$ $a_i \bar{b}_i + a_i c_i + \bar{b}_i c_i$

2. (6 points) Design the network N by giving a Boolean expression for f.


$f =$ $\bar{c}_4 (\bar{x}y) + c_4 (\bar{x} + y)$

Problem 5 (17 points)


Shown below is an 8-bit arithmetic unit (AU) which operates on two 8-bit 2's complement numbers A and B. Each network N computes a^* and b^* , where:

$$a^* = k_1' k_0' + k_1 a$$
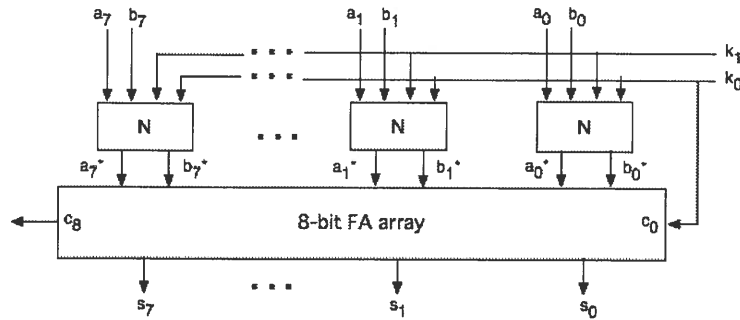
$$b^* = k_1 k_0' b' + k_0 b + k_1' k_0' a$$



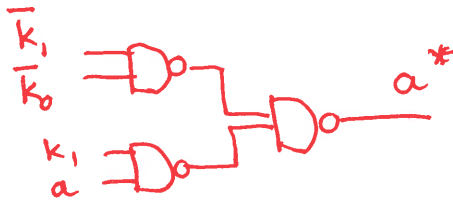1. (4 points) Give a 2-level NAND gate implementation of a^* . Assume complemented inputs are available.




2. (13 points) Complete the table below.
- Give the values for a^* , b^* , c_0
 - Specify the operation performed. Express your answer as an arithmetic function (PLUS/MINUS) of A and B (e.g., "a plus the complement of b" is not an appropriate response).

k_1	k_0	a^*	b^*	c_0	Operation performed as a function of A and B (e.g. A PLUS/MINUS B)
0	0	1	a	0	A MINUS 1
0	1	0	b	1	B PLUS 1
1	0	a	b'	0	A MINUS B MINUS 1
1	1	a	b	1	A PLUS B PLUS 1

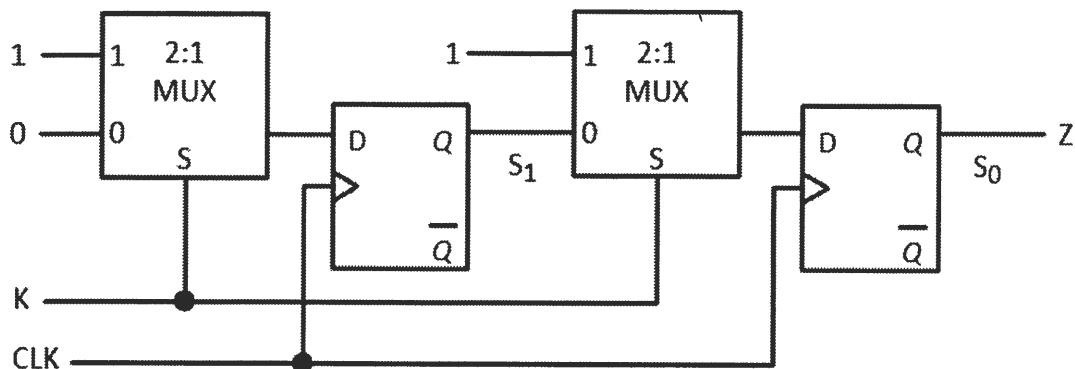Problem 6 (12 points): Finite State Machines



The circuit below is a 2-bit register that shifts right with serial input of 0 when $K=0$ and parallel loads with inputs of 1 when $K=1$.



1. (6 points) Complete the state transition table for the circuit.

S_1	S_0	K	S_1^+	S_0^+	Z
0	0	0	0	0	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	1	1
1	1	1	1	1	1

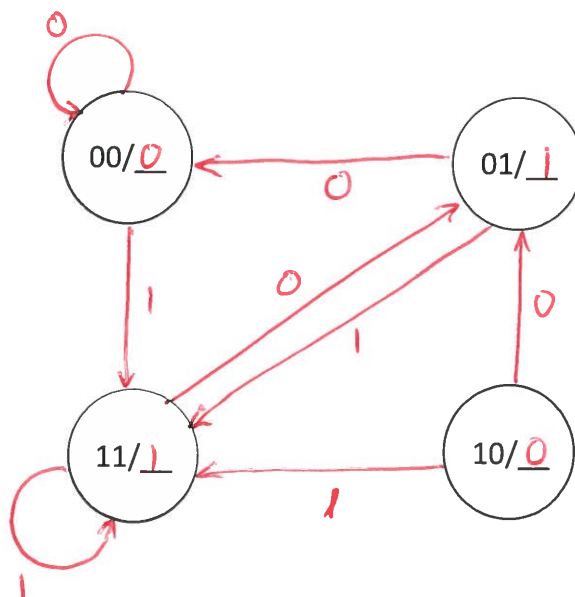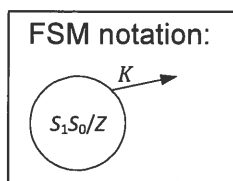2. (6 points) Complete the state transition diagram for the circuit.



Boolean algebra properties

Commutativity	$x \cdot y = y \cdot x$	$x + y = y + x$
Associativity	$(x \cdot y) \cdot z = x \cdot (y \cdot z)$	$(x + y) + z = x + (y + z)$
Distributivity	$x \cdot (y + z) = x \cdot y + x \cdot z$	$x + y \cdot z = (x + y) \cdot (x + z)$
Idempotence	$x \cdot x = x$	$x + x = x$
Identity	$x \cdot 1 = x$	$x + 0 = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$
Complementarity	$x \cdot x' = 0$	$x + x' = 1$
Involution		$(x')' = x$
DeMorgan's	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$
Absorption	$x \cdot (x + y) = x$	$x + x \cdot y = x$
No-Name	$x \cdot (x' + y) = x \cdot y$	$x + x' \cdot y = x + y$
Consensus	$(x+y) \cdot (y+z) \cdot (x'+z) =$ $(x+y) \cdot (x'+z)$	$x \cdot y + y \cdot z + x' \cdot z =$ $x \cdot y + x' \cdot z$

Feel free to tear this page off and use it as scratch paper.