

**ECE 120 Third Midterm Exam  
Fall 2016**

Tuesday, November 15, 2016

Name:	SOLUTIONS	NetID:	
Discussion Section:			
9:00 AM			
10:00 AM			
11:00 AM	<input type="checkbox"/> AB1	<input type="checkbox"/> AB8	
12:00 PM	<input type="checkbox"/> AB2	<input type="checkbox"/> AB9	
1:00 PM	<input type="checkbox"/> AB3	<input type="checkbox"/> ABA	
2:00 PM	<input type="checkbox"/> AB4	<input type="checkbox"/> ABB	
3:00 PM	<input type="checkbox"/> AB5		
4:00 PM	<input type="checkbox"/> AB6	<input type="checkbox"/> ABC	
5:00 PM	<input type="checkbox"/> AB7	<input type="checkbox"/> ABD	

- **Be sure that your exam booklet has 8 pages.**
- **Write your name, netid and check discussion section on the title page.**
- **Do not tear the exam booklet apart, except for the last two pages.**
- **Use backs of pages for scratch work if needed.**
- **This is a closed book exam. You may not use a calculator.**
- **You are allowed one handwritten 8.5 x 11" sheet of notes (both sides).**
- **Absolutely no interaction between students is allowed.**
- **Clearly indicate any assumptions that you make.**
- **The questions are not weighted equally. Budget your time accordingly.**
- **Show your work.**

Problem 1	16 points	_____
Problem 2	23 points	_____
Problem 3	15 points	_____
Problem 4	10 points	_____
Problem 5	16 points	_____

---

Total	80 points	_____
-------	-----------	-------

**Problem 1 (16 points): FSM Design**


In this problem you will implement a **011** sequence recognizer. The circuit has one input  $x$ , one output  $y$ , and the output is 1 if and only if the pattern **011** has been detected in the input stream.

Example:


Input:  $x = 0\ 0\ 0\ 0\ 0\ 1\ 0\ 1\ 0\ 0\ 1\ 1\ 1\ 0\ 0\ 1\ 0\ 1\ 1\ 0\ 1\ 1\ 1\ \dots$   
 Output:  $y = 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ 0\ 0\ 0\ 0\ 0\ 1\ 0\ 0\ 1\ 0\ \dots$

Note that the output sequence is delayed by 1 clock cycle compared to the input sequence because the output is a function of the flip-flop outputs.

 
- (11 points)** Draw the *Moore* state diagram, labeling the output and inputs. Give the meaning of each state.



State	Meaning
"Start" 00	Nothing seen
01	'0' seen
10	'01' seen
11	'011' seen

 

 - (5 points)** Shown below is a 4-bit shift register, constructed with 4 positive-edge-triggered D flip-flops. Use this shift register and **only one gate** (NOT, AND, OR, NAND, NOR, XOR, or XNOR) to implement a circuit which recognizes **011** just like the example at the top of the page. Be sure to label input  $x$  and output  $y$ .




**Problem 2 (23 points): FSM Analysis**

1. (13 points) The 3-bit binary up counter shown to the right has parallel load. If  $LOAD=1$ , the counter loads the input value  $L_2L_1L_0$  into  $Q_2Q_1Q_0$  in the next clock cycle; if  $LOAD=0$ ,  $Q_2Q_1Q_0$  counts up.

Fill out the state-transition table below for state  $S_2S_1S_0$ . Start by filling out the  $LOAD$  column.


$S_2$	$S_1$	$S_0$	LOAD	$S_2^+$	$S_1^+$	$S_0^+$
0	0	0	1	0	1	0
0	0	1	1	1	1	0
0	1	0	0	0	1	1
0	1	1	0	1	0	0
1	0	0	1	1	0	1
1	0	1	1	0	0	1
1	1	0	0	1	1	1
1	1	1	0	0	0	0

 

 2. (10 points) In this part, we use a 3-bit modulo-6 binary up counter  $Q_2Q_1Q_0$  (not shown in the figure) to light up the 7-segment LED display shown to the right. For example, the segment marked 'A' lights up if the input  $A=1$ .

In the table below, the sequence of states  $Q_2Q_1Q_0$  generated by the counter is given to you, starting with the state 001 in clock cycle #1.


Fill in the LED segments that light up in each clock cycle. The first one has been done for you.



cycle	#1	#2	#3	#4	#5	#6
$Q_2Q_1Q_0$	001	010	011	100	101	000
seven segment display						

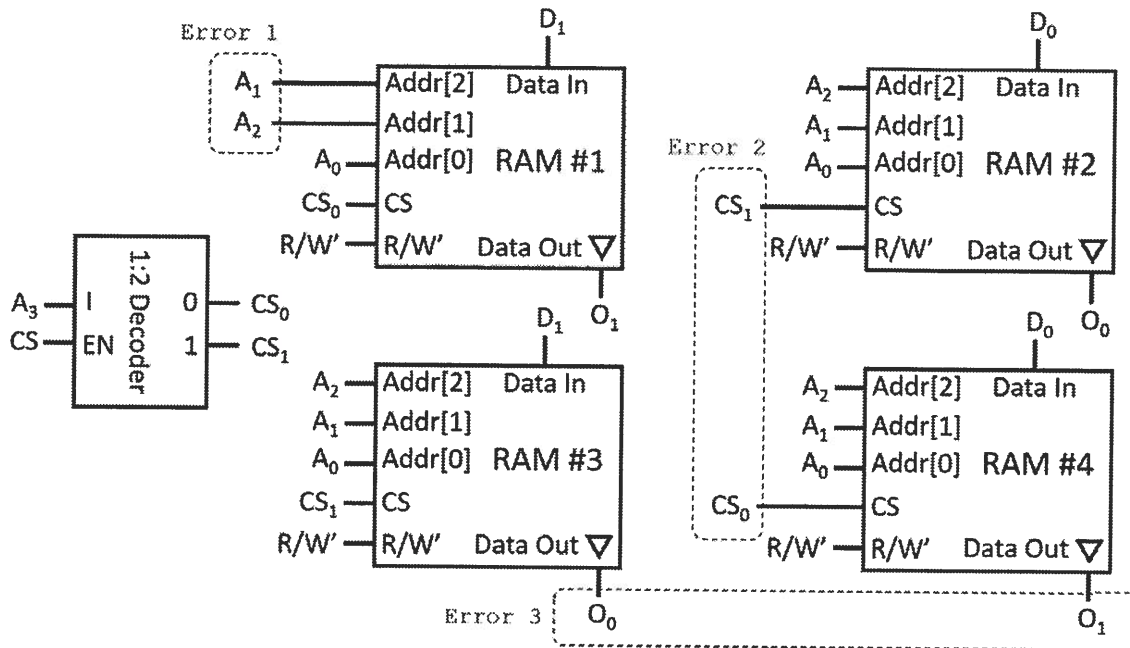**Problem 3 (15 points): Memory**

A careless engineer attempted to build a 16x2 RAM out of a 1:2 decoder and four 8x1 RAMs. The 16x2 RAM is intended to have two Data-In bits  $D_1D_0$ , four address bits  $A_3A_2A_1A_0$ , chip select  $CS$ , read/not-write  $R/W'$ , and two Data-Out bits  $O_1O_0$ . Unfortunately, the engineer switched 3 pairs of connections compared to the conventional design. The mistakes are shown in the diagram as Errors 1 to 3.



1. (12 points) Suppose a user attempts to write ( $CS=1$  and  $R/W'=0$ ) into the faulty 16x2 RAM with data  $D_1D_0 = 01$  at address  $A_3A_2A_1A_0 = 0101$ . Indicate in the table below which of the 8x1 RAMs are accessed by circling YES or NO for each RAM. If an 8x1 RAM is accessed, also write down the 1-bit Data-In and the 3-bit address  $Addr[2:0]$  for that 8x1 RAM.

RAM #1	Accessed? YES / NO	RAM #2	Accessed? YES / NO
Data-In 0	Addr[2:0] 011	Data-In	Addr[2:0]
RAM #3	Accessed? YES / NO	RAM #4	Accessed? YES / NO
Data-In	Addr[2:0]	Data-In 1	Addr[2:0] 101

2. (3 points) If you want to make a functional 16x2 RAM by correcting the minimal number of errors, which error(s) must you fix?

Circle the error(s) that MUST be fixed: Error 1 Error 2 Error 3

**Problem 4 (10 points): von Neumann Model**

For each question, **CIRCLE EXACTLY ONE ANSWER.**

In the von Neumann model, where is the program stored?

processing  
unit

output

MAR

PC

memory

What is the first step of instruction processing in a computer based on the von Neumann model?

EXECUTE

READ  
OPERANDS

DECODE

FETCH

INCREMENT  
PC

Operands for instructions in a computer based on the von Neumann model **can NOT be found** in which of the following?

memory

tri-state  
buffers

register  
file

input

PC

Which of the following contains the address of the next instruction to be executed by the computer?

ALU

MDR

PC

IR

MAR

In the von Neumann model, the memory includes which of the following?

MAR

register  
file

KBDR

FSM

control  
unit

### Problem 5 (16 points): LC-3 Interpretation and Assembly

The registers of an LC-3 processor currently have the values shown in the table to the right.

R0	x0111	R4	bits	PC	x3001
R1	x3002	R5	bits	IR	xE622
R2	x1175	R6	bits	MAR	x3000
R3	x3023	R7	bits	MDR	xE622

The table to the right shows some of the contents of the LC-3 processor's memory.

address	contents	RTL interpretation
x3000	1110 0110 0010 0010	R3 ← PC + x0022
x3001	0110 0010 1100 0001	R1 ← M[R3 + 1]
x3002	1001 0100 0111 1111	R2 ← NOT R1
x3003	0111 0100 1100 0010	M[R3 + 2] ← R2
	...	...
x3023	0000 1111 0000 0101	PC ← PC + xFF05
x3024	0001 0011 0001 0100	(data: x1314)
x3025	1101 1010 1011 1100	(data: xDABC)
x3026	0000 0000 0000 0000	(no operation)

When the bits represent instructions, an interpretation has been provided for you in RTL.

Here's the question:

The LC-3 processor **PROCESSES THREE INSTRUCTIONS.**

1. (7 points) Write a complete list of the sequence of values taken by the MAR register as the LC-3 processes these instructions. Use only as many lines as are necessary.

#1: x3000 (initial value)      #5: x3003  
 #2: x3001      #6: x3025  
 #3: x3024      #7: \_\_\_\_\_  
 #4: x3002      #8: \_\_\_\_\_

2. (9 points) Complete the tables below with the **FINAL** values (after processing of three instructions) of each register and memory location. If you cannot know a particular value, write "bits." *Note: You must write your answers in hexadecimal.*


R0	x0111	PC	x3004	memory address	contents
R1	x1314	IR	x74C2	x3002	x947F
...	...	MDR	xECEB	...	...
R4	bits			x3024	x1314
				x3025	xECEB

LC-3 Instructions


NOTES: RTL corresponds to execution (after fetch!); JSRR not shown

ADD	0001	DR	SR1	0	00	SR2	ADD DR, SR1, SR2	LD	0010	DR	PCoffset9	LD DR, PCoffset9	
							$DR \leftarrow SR1 + SR2, Setcc$					$DR \leftarrow M[PC + SEXT(PCoffset9)], Setcc$	
ADD	0001	DR	SR1	1	imm5		ADD DR, SR1, imm5	LDI	1010	DR	PCoffset9	LDI DR, PCoffset9	
							$DR \leftarrow SR1 + SEXT(imm5), Setcc$					$DR \leftarrow M[M[PC + SEXT(PCoffset9)]], Setcc$	
AND	0101	DR	SR1	0	00	SR2	AND DR, SR1, SR2	LDR	0110	DR	BaseR	offset6	LDR DR, BaseR, offset6
							$DR \leftarrow SR1 \text{ AND } SR2, Setcc$						$DR \leftarrow M[BaseR + SEXT(offset6)], Setcc$
AND	0101	DR	SR1	1	imm5		AND DR, SR1, imm5	LEA	1110	DR	PCoffset9	LEA DR, PCoffset9	
							$DR \leftarrow SR1 \text{ AND } SEXT(imm5), Setcc$						$DR \leftarrow PC + SEXT(PCoffset9), Setcc$
BR	0000	n	z	p	PCoffset9		BR{nzp} PCoffset9	NOT	1001	DR	SR	111111	NOT DR, SR
							$((n \text{ AND } N) \text{ OR } (z \text{ AND } Z) \text{ OR } (p \text{ AND } P))$ $PC \leftarrow PC + SEXT(PCoffset9)$						$DR \leftarrow \text{NOT } SR, Setcc$
JMP	1100	000	BaseR	000000			JMP BaseR	ST	0011	SR	PCoffset9	ST SR, PCoffset9	
							$PC \leftarrow BaseR$						$M[PC + SEXT(PCoffset9)] \leftarrow SR$
JSR	0100	1	PCoffset11				JSR PCoffset11	STI	1011	SR	PCoffset9	STI SR, PCoffset9	
							$R7 \leftarrow PC, PC \leftarrow PC + SEXT(PCoffset11)$						$M[M[PC + SEXT(PCoffset9)]] \leftarrow SR$
TRAP	1111	0000	trapvect8				TRAP trapvect8	STR	0111	SR	BaseR	offset6	STR SR, BaseR, offset6
							$R7 \leftarrow PC, PC \leftarrow M[ZEXT(trapvect8)]$						$M[BaseR] + SEXT(offset6) \leftarrow SR$

LC-3 FSM

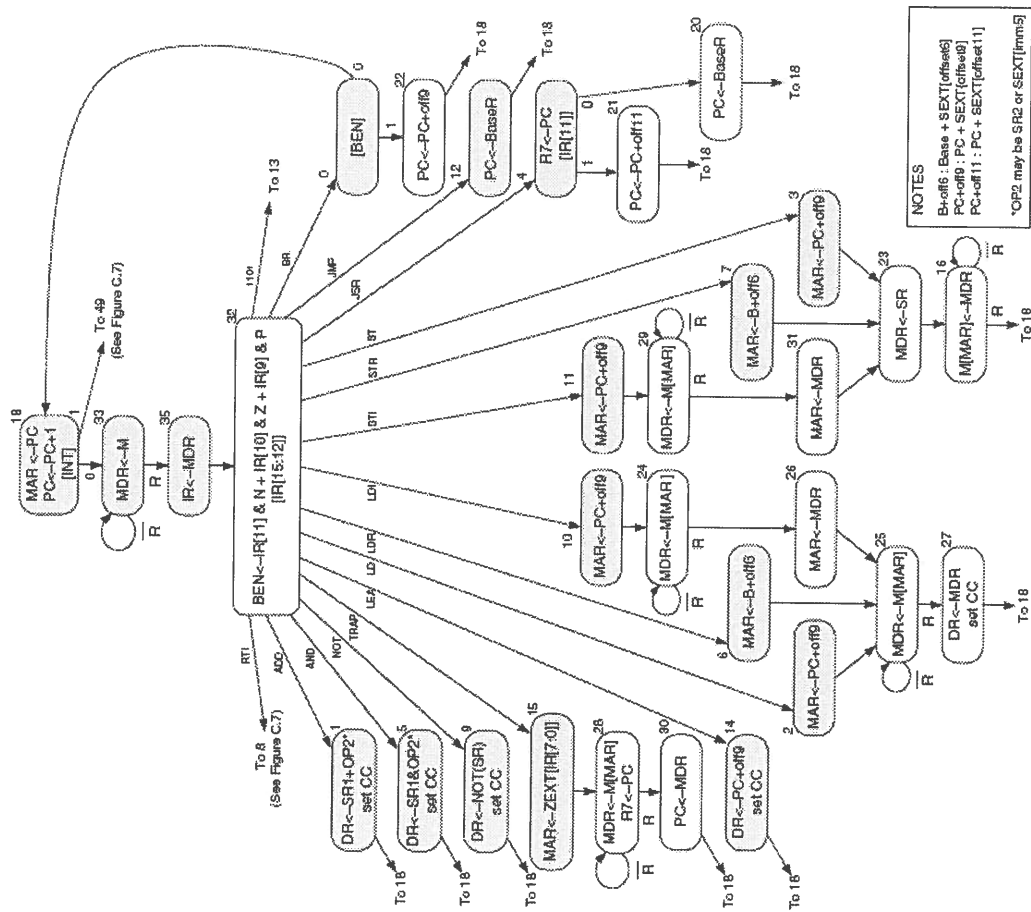

LC-3 Datapath

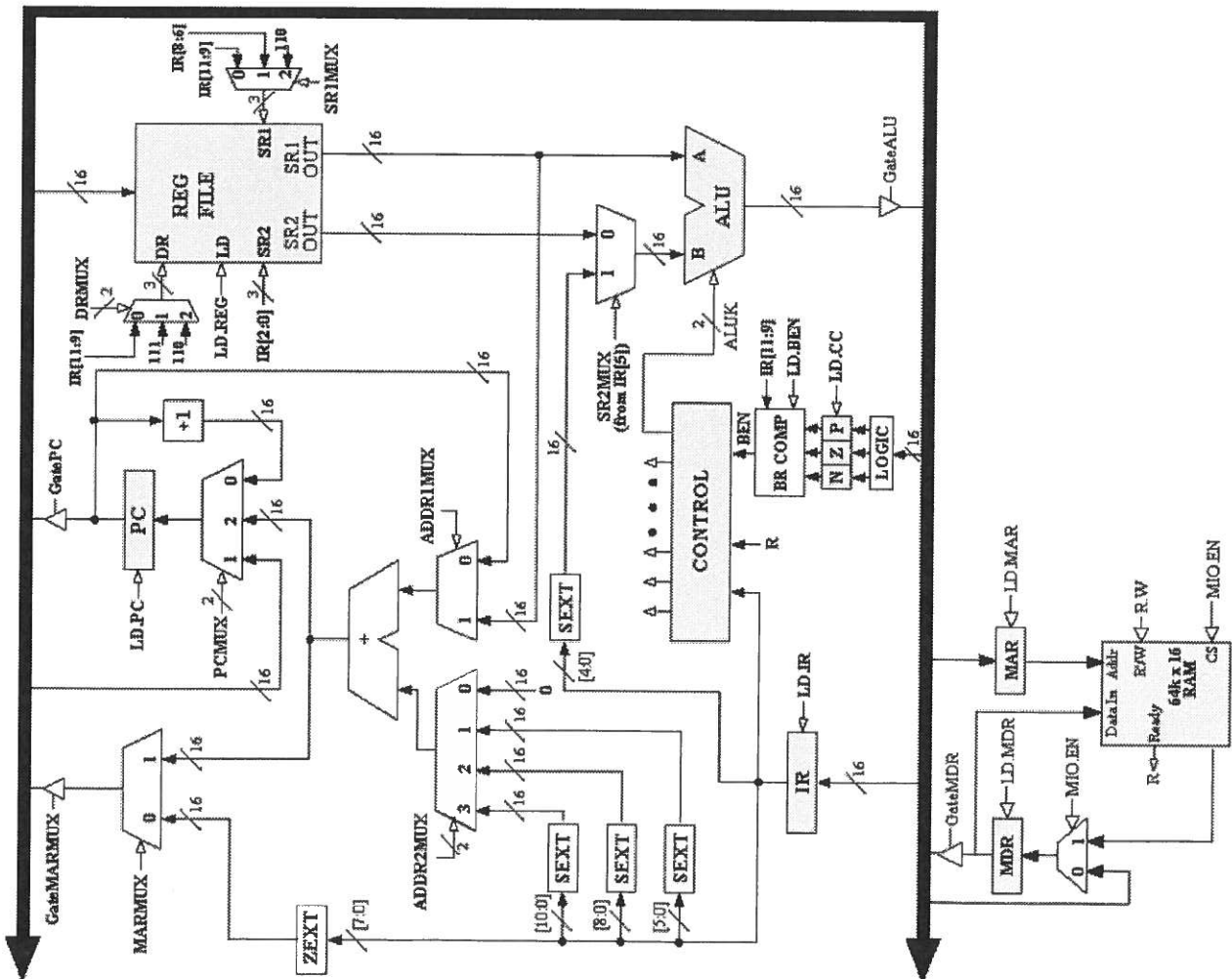

LC-3 Datapath Control Signals

Signal	Description	Signal	Description
LD.MAR = 1, MAR is loaded		LD.CC = 1, updates status bits from system bus	
LD.MDR = 1, MDR is loaded		GateMARMUX = 1, MARMUX output is put onto system bus	
LD.IR = 1, IR is loaded		GateMDR = 1, MDR contents are put onto system bus	
LD.PC = 1, PC is loaded		GateALU = 1, ALU output is put onto system bus	
LD.REG = 1, register file is loaded		GatePC = 1, PC contents are put onto system bus	
LD.BEN = 1, updates Branch Enable (BEN) bit			
MARMUX {	<ul style="list-style-type: none"> <li>= 0, chooses ZEXT IR[7:0]</li> <li>= 1, chooses address adder output</li> </ul>	MIO.EN {	<ul style="list-style-type: none"> <li>= 1, Enables memory, chooses memory output for MDR input</li> <li>= 0, Disables memory, chooses system bus for MDR input</li> </ul>
ADDR1MUX {	<ul style="list-style-type: none"> <li>= 0, chooses PC</li> <li>= 1, chooses reg file SR1 OUT</li> </ul>	R.W {	<ul style="list-style-type: none"> <li>= 1, M[MAR]&lt;-MDR when MIO.EN = 1</li> <li>= 0, MDR&lt;-M[MAR] when MIO.EN = 1</li> </ul>
ADDR2MUX {	<ul style="list-style-type: none"> <li>= 00, chooses "0...00"</li> <li>= 01, chooses SEXT IR[5:0]</li> <li>= 10, chooses SEXT IR[8:0]</li> <li>= 11, chooses SEXT IR[10:0]</li> </ul>	ALUK {	<ul style="list-style-type: none"> <li>= 00, ADD</li> <li>= 01, AND</li> <li>= 10, NOT A</li> <li>= 11, PASS A</li> </ul>
PCMUX {	<ul style="list-style-type: none"> <li>= 00, chooses PC + 1</li> <li>= 01, chooses system bus</li> <li>= 10, chooses address adder output</li> </ul>	DRMUX {	<ul style="list-style-type: none"> <li>= 00, chooses IR[11:9]</li> <li>= 01, chooses "111"</li> <li>= 10, chooses "110"</li> </ul>
SR1MUX {	<ul style="list-style-type: none"> <li>= 00, chooses IR[11:9]</li> <li>= 01, chooses IR[8:6]</li> <li>= 10, chooses "110"</li> </ul>		