

**ECE 120 Third Midterm Exam
Spring 2016**

Tuesday, April 19, 2016

Name:

SOLUTIONS

NetID:

Discussion Section:

9:00 AM	[] AB1	
10:00 AM	[] AB2	
11:00 AM	[] AB3	
12:00 PM	[] AB4	
1:00 PM	[] AB5	[] ABA
2:00 PM	[] AB6	
3:00 PM	[] AB7	[] ABB
4:00 PM	[] AB8	[] ABC
5:00 PM	[] AB9	[] ABD

- Be sure that your exam booklet has 8 pages.
- Write your name, netid and check discussion section on the title page.
- Do not tear the exam booklet apart.
- Use backs of pages for scratch work if needed.
- This is a closed book exam. You may not use a calculator.
- You are allowed one handwritten 8.5 x 11" sheet of notes (both sides).
- Absolutely no interaction between students is allowed.
- Clearly indicate any assumptions that you make.
- The questions are not weighted equally. Budget your time accordingly.
- Show your work.

Problem 1 19 points _____

Problem 2 18 points _____

Problem 3 22 points _____

Problem 4 15 points _____


Problem 5 26 points _____

Total 100 points _____

Problem 1 (19 points): Memory

 1. (12 points) Complete the logic diagram below for this 256×8 RAM constructed from 32×4 RAMs. **Clearly label all wires and components.** Specifically:

- Give the size of the decoder and label its inputs and outputs.
- Draw and label the address lines. *E.g. use $A[3:0]$ notation.*
- Draw the CS input lines to the 32×4 RAMs.



2. (7 points) Consider a 32×32 RAM constructed using 16×8 RAM chips. **Note:** This part uses different RAMs than was used in part 1.

How many 16×8 RAM chip(s) are needed? 8

Specify the signal widths (number of bits) for each of the following external signals to the 32×32 RAM.

Data-In = 32 Address = 5 R/W' = 1


Problem 2 (18 points): FSM Design

In this problem you will implement a 0101 sequence recognizer. The circuit has one input x , one output z , and the output is 1 if and only if the pattern 0101 has been detected in the input stream.

Example:

Input: $x = 0 \ 0 \ 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \dots$
Output: $z = 0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \ 0 \ 1 \ 0 \ 0 \ 0 \dots$

 1. (10 points) Draw the *Moore state diagram*, using as few states as possible. Label the states A, B, C, etc. and give the meaning of each state.




State	Meaning
A	- recognized
B	0 "
C	01 "
D	010 "
E	0101 "

2. (3 points) What is the **minimum** number of flip-flops needed to implement your circuit from part 1?

Answer


3

 3. (5 points) Shown below is a 5-bit **shift register**, constructed with 5 positive-edge-triggered D flip-flops. Use this shift register and **only one gate** to implement a circuit which recognizes 0101 just like the example at the top of the page. Be sure to label input x and output z .



 Problem 3 (22 points): FSM Circuit Analysis

The circuit below shows a 3-bit synchronous counter constructed using 3 negative-edge-triggered T flip-flops.




1. (5 points) Give Boolean expressions for the T_2 , T_1 , T_0 flip-flop inputs, each as a function of the state variables Q_2 , Q_1 , Q_0 .

$$T_2 = \underline{Q_2 Q_0 + Q_1 Q_0} \quad T_1 = \underline{Q_0 \bar{Q}_2} \quad T_0 = \underline{1}$$

2. (9 points) Complete the following table.

Current State			Flip-Flop Inputs			Next State		
Q_2	Q_1	Q_0	T_2	T_1	T_0	Q_2^+	Q_1^+	Q_0^+
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	0	0	1	0	1	1
0	1	1	1	1	1	1	0	0
1	0	0	0	0	1	1	0	1
1	0	1	1	0	1	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	0	1	0	1	0

 3. (5 points) Complete the state transition diagram.



4. (3 points) Assuming the start state is $Q_2 Q_1 Q_0 = 000$, in what sequence does this counter count?

$$\textcircled{0} \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 4 \rightarrow 5 \rightarrow$$

Problem 4 (15 points): Von Neumann model

1. (5 points) Which phase(s) of the instruction cycle access memory when processing the LEA instruction? Circle **ALL correct** answers. If a phase is not used at all in processing this instruction, *don't circle it.*

 FETCH

DECODE

EVALUATE ADDRESS

FETCH OPERANDS

EXECUTE

STORE RESULT

2. (5 points) Which component(s) of the Von Neumann model are involved in processing the JMP instruction? Processing includes all phases of the instruction cycle. Circle **ALL correct** answers.

 MEMORY PROCESSING UNIT CONTROL UNIT

INPUT

OUTPUT

3. (5 points) Which component(s) of the Von Neumann model set the GatePC signal in the LC-3 datapath? Circle **ALL correct** answers.

MEMORY

PROCESSING UNIT

 CONTROL UNIT

INPUT

OUTPUT

Problem 5 (26 points): LC-3 instructions

The following LC-3 program fragment, represented as four hexadecimal numbers, is stored in memory at the indicated locations and the following values are stored in registers:

Address	Instruction
x3FFF	xAFFE
x4000	x2001
x4001	x743F
x4002	x3002

Register	Value
R0	xF021
R1	xF023
R2	xF025
R3	xF027


1. (12 points) Complete the following table. (Refer to the LC-3 handout at the end of the exam.)

Address	Instruction	Binary instruction	RTL (Be specific to this instruction)
x3FFF	xAFFE	1010 111 111111110	$R7 \leftarrow M[M[PC - 2]]$ setcc
x4000	x2001	0010 000 000000001	$R0 \leftarrow M[PC+1]$ setcc
x4001	x743F	0111 010 000 11111	$M[R0-1] \leftarrow R2$
x4002	x3002	0011 000 000000010	$M[PC+2] \leftarrow R0$

2. (14 points) Assuming PC is initially set to x4000, trace the execution of the given program segment for two instruction cycles, filling in the table below. Write down the values stored in the PC, IR, MAR, MDR, R0, N, Z, and P registers at the end of each instruction cycle. Values for PC, IR, MAR, MDR, and R0 should be written in *hexadecimal*. Values for N, Z, and P should be written in *binary*.

PC	IR	MAR	MDR	R0	N	Z	P
x4001	x2001	x4002	x3002	x3002	0	0	1
x4002	x743F	x3001	xF025	x3002	0	0	1

LC-3 FSM

 

NOTES: RTL corresponds to execution (after fetch!); JSRR not shown

ADD	0001	DR	SR1	0	00	SR2	ADD DR, SR1, SR2	LD	0010	DR	PCoffset9	LD DR, PCoffset9
DR \leftarrow SR1 + SR2, Setcc							DR \leftarrow M[PC + SEXT(PCoffset9)], Setcc					
ADD	0001	DR	SR1	1		imm5	ADD DR, SR1, imm5	LDI	1010	DR	PCoffset9	LDI DR, PCoffset9
DR \leftarrow SR1 + SEXT(imm5), Setcc							DR \leftarrow M[M[PC + SEXT(PCoffset9)]], Setcc					
AND	0101	DR	SR1	0	00	SR2	AND DR, SR1, SR2	LDR	0110	DR	BaseR	LDR DR, BaseR, offset6
DR \leftarrow SR1 AND SR2, Setcc							DR \leftarrow M[BaseR + SEXT(offset6)], Setcc					
AND	0101	DR	SR1	1		imm5	AND DR, SR1, imm5	LEA	1110	DR	PCoffset9	LEA DR, PCoffset9
DR \leftarrow SR1 AND SEXT(imm5), Setcc							DR \leftarrow PC + SEXT(PCoffset9), Setcc					
BR	0000	n	z	p			BR{nzp} PCoffset9	NOT	1001	DR	SR	NOT DR, SR
((n AND N) OR (z AND Z) OR (p AND P)): PC \leftarrow PC + SEXT(PCoffset9)							DR \leftarrow NOT SR, Setcc					
JMP	1100	000	BaseR		0000000		JMP BaseR	ST	0011	SR	PCoffset9	ST SR, PCoffset9
PC \leftarrow BaseR							M[PC + SEXT(PCoffset9)] \leftarrow SR					
JSR	0100	1			PCoffset11		JSR PCoffset11	STI	1011	SR	PCoffset9	STI SR, PCoffset9
R7 \leftarrow PC, PC \leftarrow PC + SEXT(PCoffset11)							M[M[PC + SEXT(PCoffset9)]] \leftarrow SR					
TRAP	1111	0000			trapvect8		TRAP trapvect8	STR	0111	SR	BaseR	STR SR, BaseR, offset6
R7 \leftarrow PC, PC \leftarrow M[ZEXT(trapvect8)]							M[BaseR + SEXT(offset6)] \leftarrow SR					

LC-3 Datapath Control Signals

Signal	Description
LD.MAR = 1, MAR is loaded	LD.MAR = 1, updates status bits from system bus
LD.IR = 1, IR is loaded	LD.IR = 1, PC is loaded
LD.PC = 1, PC is loaded	LD.PC = 1, register file is loaded
LD.BEN = 1, updates Branch Enable (BEN) bit	LD.BEN = 1, updates Branch Enable (BEN)
GateMARMUX = 1, MARMUX output is put onto system bus	GateMARMUX = 1, PC contents are put onto system bus
GateALU = 1, ALU output is put onto system bus	GateALU = 1, ALU output is put onto system bus
GatePC = 1, PC output is put onto system bus	GatePC = 1, PC output is put onto system bus
MARMUX = 0, chooses memory, MIO.EN = 1	MARMUX = 0, chooses memory, MIO.EN = 1
MARMUX = 1, chooses memory, MIO.EN = 0	MARMUX = 1, chooses memory, MIO.EN = 0
ADDRIOMUX = 0, chooses PC + 1	ADDRIOMUX = 0, chooses PC + 1
ADDRIOMUX = 1, chooses SEXT IR[5:0]	ADDRIOMUX = 1, chooses SEXT IR[5:0]
PCMUX = 00, chooses "0...00"	PCMUX = 00, chooses "0...00"
PCMUX = 01, chooses SEXT IR[8:6]	PCMUX = 01, chooses SEXT IR[8:6]
PCMUX = 10, chooses address bus	PCMUX = 10, chooses address bus
PCMUX = 11, chooses SEXT IR[10:0]	PCMUX = 11, chooses SEXT IR[10:0]
PCMUX = 10, chooses PC + 1	PCMUX = 10, chooses PC + 1
PCMUX = 11, chooses SEXT IR[7:0]	PCMUX = 11, chooses SEXT IR[7:0]
ADDR1MUX = 0, chooses reg file SR1 OUT	ADDR1MUX = 0, chooses reg file SR1 OUT
ADDR1MUX = 1, chooses address adder output	ADDR1MUX = 1, chooses address adder output
ADDR2MUX = 0, chooses SEXT IR[5:0]	ADDR2MUX = 0, chooses SEXT IR[5:0]
ADDR2MUX = 1, chooses SEXT IR[8:6]	ADDR2MUX = 1, chooses SEXT IR[8:6]
DRMUX = 00, chooses "0...00"	DRMUX = 00, chooses "0...00"
DRMUX = 01, chooses "111"	DRMUX = 01, chooses "111"
DRMUX = 10, chooses "110"	DRMUX = 10, chooses "110"
DRMUX = 11, chooses "100"	DRMUX = 11, chooses "100"
ALUK = 00, ADD	ALUK = 00, ADD
ALUK = 01, AND	ALUK = 01, AND
ALUK = 10, NOT A	ALUK = 10, NOT A
ALUK = 11, PASS A	ALUK = 11, PASS A
R.W = 0, MDR<-MAR when MIO.EN = 1	R.W = 0, MDR<-MAR when MIO.EN = 1
R.W = 1, MAR<-MDR when MIO.EN = 1	R.W = 1, MAR<-MDR when MIO.EN = 1
MIO.EN = 0, Disables memory, chooses system bus for MDR input	MIO.EN = 0, Disables memory, chooses system bus for MDR input
MIO.EN = 1, Enables memory, chooses memory, chooses system bus for MDR input	MIO.EN = 1, Enables memory, chooses memory, chooses system bus for MDR input
SEXT = 0, 1, 2, 3, 4, 5, 6, 7	SEXT = 0, 1, 2, 3, 4, 5, 6, 7
ZEXT = 0, 1, 2, 3, 4, 5, 6, 7	ZEXT = 0, 1, 2, 3, 4, 5, 6, 7

Figure 4-10 LC-3 Datapath

