

Homework 7


i Homework 7 is due on Wednesday, April 8, at the start of the lecture. Remember to include your *Discussions section* (e.g. ED1) and follow the complete Homework submission guidelines.

Please ask all questions about this assignment during the office hours, or post them on [piazza](#).

Sequential logic elements and serialization

 1. Circuits with feedback loop

This question pertains to the following circuit.



a. Complete the next-state table for the latch circuit shown above and express next state Q^+ as a function of C , $DATA$, and current state Q .



C	DATA	Q^+
0	0	
0	1	
1	0	
1	1	

b. Can this circuit store a bit? Explain your answer in terms of the above truth table.

  2. Master Slave Flip Flop

Review the two master-slave flip flop designs below. They both are implemented with gated D latches. (NOTE: WE stands for write enable.)


- Express next -state output Q^+ of the *master* gated D latch as a function of inputs D_m , $CLOCK$, and its current state Q for both circuits.
- Express next -state output Q^+ of the *slave* gated D latch as a function of inputs D_s , $CLOCK$, and its current state Q for both circuits.
- Compare the behavior of the two circuits, and explain the major difference in their functionality.



3. Registers


Complete the design of a 3-bit register that performs the operations listed in the table below. Parallel load inputs should be labeled and indexed as P_i . Serial load inputs should be labeled and indexed as C_i . Function selection should be labeled F_i . When arithmetic operations are performed, assume that the numbers are in 2's complement representation. You may use Q_i inputs without drawing the wire from the outputs of the flip flops (just write the appropriate Q_i label).

F1	F0	Operation
0	0	Parallel load register
0	1	Logical shift left
1	0	Arithmetic shift right
1	1	Circular shift left

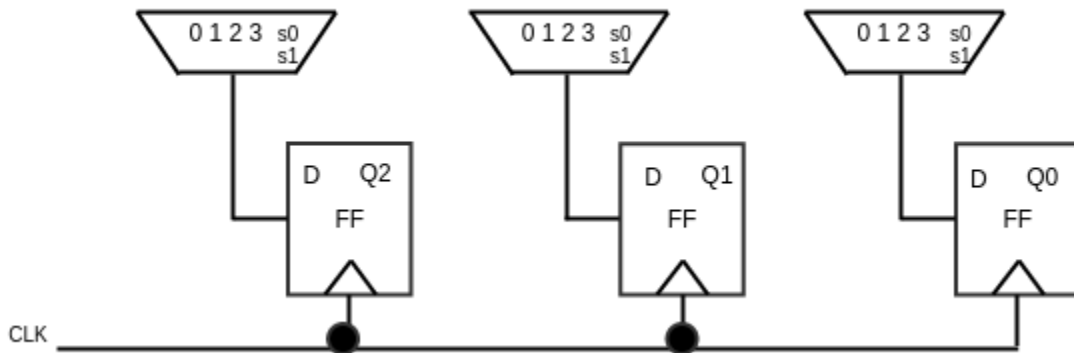


 4. Shift Registers


Draw the timing diagrams for Q_0 , Q_1 , Q_2 and Q_3 for the two circuits below (for the 4 clock cycles shown below). Assume all the Q_i outputs are at low state at the beginning.



(a)

 


(b)

 

 5. Odd number of 1s checking using serialization


Shown below is a circuit that checks whether the n -bit input $A = a_{n-1} \dots a_1 a_0$ contains an odd number of 1s in its binary representation. The circuit produces an output p_n of 0 if the number of 1s is even, or produces an output p_n of 1 otherwise. In homework 6, you already designed each of the Unit Bit Slices as *identical circuits*.



Re-implement this bit-sliced design using *serialization* approach presented in Prof. Lumetta's notes set 3.1. **Do NOT redraw the gate-level implementation of a Unit Bit Slice from homework 6.** Instead use a box called Unit Bit Slice as a building block and add the storage and logic necessary to turn the bit-sliced design into a serial implementation. Assume that you have an input F to make sure that the Unit Bit Slice starts with the correct data. F is 1 when a_0 enters the Unit Bit Slice and it is 0 at all other times.

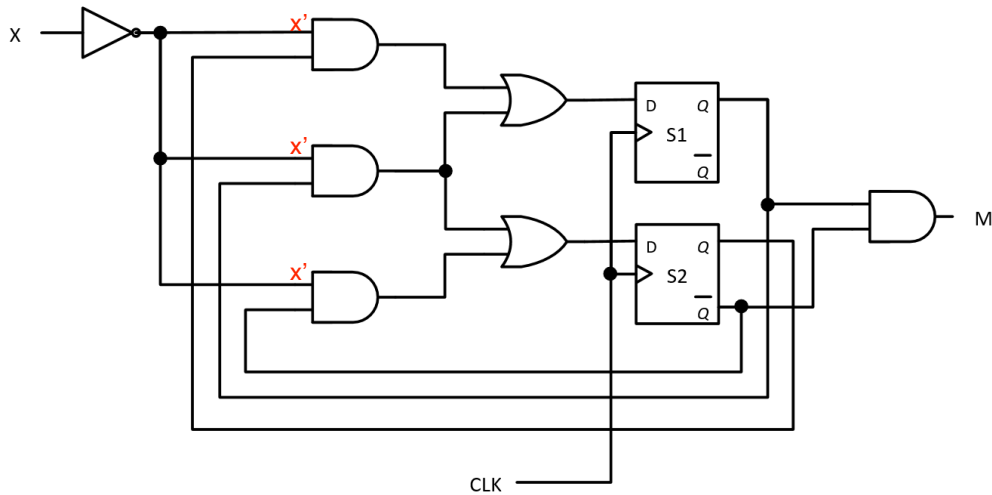6. Analyzing sequential circuits

Below is an implementation for a sequential circuit, with X as input, and M as the output.



Derive Boolean expressions for next states S_1^+ , S_2^+ , and output M (based on S_1 , S_2 and input X).

7. Programming

Download, compile, and execute the program [latch.c](#). The program finds and prints all stable states for an R'-S'-latch. Read the program and examine its output to make sure that you understand how it works.

1. Modify the program to compute stable states for two cross-coupled AND gates. In other words, replace the two NAND calculations with AND. Execute the program to find the stable states of such a circuit. For this part, you may turn in either a printed or a handwritten copy of the output (the list of states).
2. For which combination of inputs R' and S' does the "latch" that you simulated in **part (1)** have two stable states?
3. Since the "latch" simulated in **part (1)** has two stable states, one can use it to store a bit. Give two reasons that such a design (using two AND gates) is inferior to the R'-S'-latch (using two NAND gates) in CMOS technology. Explain your answers.