

## ECE 120: Introduction to Computing

### Logical Completeness

## Can We Count Functions?

A question for you:

**How many different Boolean functions exist for N bits of input?**

How can we find the answer?

Start by thinking about small values of **N**.

For example, **N=2**. Given **C = F(A,B)**,  
**how many choices do we have for F?**

## Two Bits of Input Can be Combined into 16 Functions

Write a truth table for **C = F(A,B)**.

But instead of filling in values,  
call the outputs **c<sub>i</sub>**.

The four **c<sub>i</sub>** values  
uniquely specify **F**.

If we change any **c<sub>i</sub>**,  
we get a different function.

We thus have **2×2×2×2 = 2<sup>4</sup> choices for F**.

A	B	C
0	0	<b>c<sub>0</sub></b>
0	1	<b>c<sub>1</sub></b>
1	0	<b>c<sub>2</sub></b>
1	1	<b>c<sub>3</sub></b>

## Three Bits of Input Can be Combined into 256 Functions

What about **N=3**:

**D = G(A,B,C)**?

We can again write  
a truth table.

And call the outputs **d<sub>i</sub>**.

Now we have  
**2<sup>8</sup> choices for G**.

Notice that **2<sup>8</sup> = 2<sup>(2<sup>3</sup>)</sup>**.

A	B	C	D
0	0	0	<b>d<sub>0</sub></b>
0	0	1	<b>d<sub>1</sub></b>
0	1	0	<b>d<sub>2</sub></b>
0	1	1	<b>d<sub>3</sub></b>
1	0	0	<b>d<sub>4</sub></b>
1	0	1	<b>d<sub>5</sub></b>
1	1	0	<b>d<sub>6</sub></b>
1	1	1	<b>d<sub>7</sub></b>

## N Bits of Input Can be Combined into Many Functions

Can we generalize to **N** bits?

Without drawing a truth table, please?

**N** bits means  $2^N$  rows in the truth table.

Thus we need  $2^N$  Boolean values (bits) to specify a function.

Thus  $2^{(2^N)}$  **possible functions on N bits.**

## We Need More Functions!

So why did we teach you only four functions?  
(AND, OR, NOT, and XOR)

Your homework for next time:

Write down and name all functions on 10 bits.

Include a truth table for each function!

## Alternate Homework: Understand Logical Completeness

Claim:

With enough 2-input AND, 2-input OR, and NOT functions, one can produce **any function on any number of variables.**

Believe me?


Proof: **by construction**

In other words, I'll show you how to produce an arbitrary function on an arbitrary number of variables.

## Compose Functions to Produce Functions on More Inputs


Let's start the proof.

What does this circuit produce?

 

A **3-input AND!**

What about this one?

 

A **4-input AND!**


## Use 2-Input Gates to Construct N-Input Gates

By induction, we build an **N**-input AND gate.

Base case (**N=2**): Use one 2-input AND.

**N+1** case (given an **N**-input AND):

 - Use one **N**-input AND
- and one 2-input AND
- to produce an (**N+1**)-input AND.



## Comments on Functional Form and Practical Value

A couple of comments before we continue...

- Functional form of the inductive proof:
  - base:  $\text{AND}_2(A, B) = \text{AND}_2(A, B)$
  - inductive step:
 
$$\text{AND}_{N+1}(A_0, \dots, A_N) = \text{AND}_2(\text{AND}_N(A_0, \dots, A_{N-1}), A_N)$$
- This approach is an existence proof, **not a practical way to build bigger gates.**

## The Claim is Now Slightly Simpler

Claim:

With enough ~~2-input AND~~, ~~2-input OR~~, and NOT functions, I can produce **any function on any number of variables**.

(For OR functions, use the same approach as we did with AND functions, replacing AND with OR.)

Let's first consider functions that

- produce an output of 1
- for exactly one combination of inputs (one row of the function's truth table).

## One AND Suffices for Functions that Output One 1

The function  $Q(A,B,C)$  is an example of such a function.

When is  $Q=1$ ?

Only when

$A=1$  AND  $B=0$  AND  $C=1$ .

Note that  $B=0$  when  $(\text{NOT } B) = 1$ .

In other words,  $Q = AB'C$ .

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

## Arbitrary Functions Require Only Two Steps

To produce **an arbitrary function** (which may produce the value 1 for more than one combination of inputs):

1. For each combination of inputs for which the function produces a 1, AND together the corresponding inputs or inverted inputs.\*
2. OR together the results of all AND functions.

\* The resulting AND is called a **minterm** on the input variables.

## A Sum-of-Products Can Express Any Function

The construction described results in a **sum-of-products** form because

- we produce each row of the truth table with an AND (product / multiplication notation)
- we produce the final function by ORing the ANDs (sum / addition notation).

The approach described is **often inefficient**, but it **always works**.

## {AND, OR, NOT} is Logically Complete

Definition: The set **{AND, OR, NOT}** is **logically complete** because, as we showed, any Boolean logic function on any number of inputs can be produced using only AND, OR, and NOT.

To show that another set is logically complete

- You need not construct arbitrary functions.
- You need only show how to construct AND, OR, and NOT.

## Why Do You Care? Abstraction!

Imagine working on a new device technology.

- Maybe it's based on DNA.
- Maybe it's based on new semiconductors.
- Maybe it's based on carbon nanotubes.
- Maybe you're still finishing your degree?!

What do you need to be able to build in order to replace the current technology?

**AND, OR, and NOT.**

Other people can then build higher layers of abstraction!

## Example: 3-input XOR

Let's build XOR as an example.

First, write the truth table.

What function produces

this row?

$A'B'C$

And this row?

$A'BC'$

And this one?

$AB'C'$

And this one?

$ABC$

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## 3-input XOR Expressed Using AND, OR, and NOT

Putting these four functions together, we obtain:

$A \text{ XOR } B \text{ XOR } C =$

$$A'B'C + A'BC' + AB'C' + ABC$$

Now we are ready to begin building devices such as adders and comparators to manipulate our representations...