

ECE 120: Introduction to Computing

Analyzing and Optimizing the Bit-Sliced Comparator

Area Heuristic for One Comparator Bit Slice is 20


Let's analyze area and delay.

How many literals? **12**

How many operators?

8 (6 AND, 2 OR)

So **area is 20.**

 


How Many Gate Delays to Z_1 ?

A to Z_1 :
2 gate delays

C_1 to Z_1 :
2 gate delays

C_0 to Z_1 :
not relevant


B to Z_1 :
2 gate delays
(ignoring NOT)

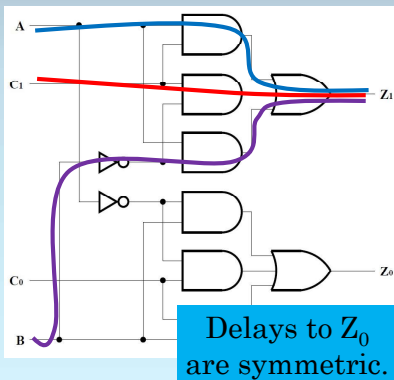

Extending from One Bit Slice to N Bit Slices

What happens in an **N-bit** design?

 
Say that **A and B are available at time 0.**



Constant Inputs are Available Arbitrarily Early

What about the 0s on the right?

 Available “forever” ... (time $-\infty$).



Use Bit Slice Timing to Calculate Times Between Slices

Now we must

- use the delays that we found for one bit slice
- to calculate times for inter-slice **C** values.


Recall that

- all **A** and **B** bits are available at **time 0**,
- so the **C to Z** delays are the most important.

We found

- **C₁ to Z₁**: 2 gate delays
- **C₀ to Z₀**: 2 gate delays

 Calculate the Time at Which C^M Becomes Available



A More Detailed Version of Our Calculations

Grey is “not relevant,” and green is maximum (time at which Z_i is available).

(bit slice 0)	A	B	C_1	C_0
input available at	0	0	$-\infty$	$-\infty$
delay from input to Z_1	+2	+2	+2	
Z_1 not available until	2	2	$-\infty$	
delay from input to Z_0	+2	+2		+2
Z_0 not available until	2	2		$-\infty$

A More Detailed Version of Our Calculations

Grey is “not relevant,” and green is maximum (time at which Z_i is available).

(bit slice 1)	A	B	C_1	C_0
input available at	0	0	2	2
delay from input to Z_1	+2	+2	+2	
Z_1 not available until	2	2	4	
delay from input to Z_0	+2	+2		+2
Z_0 not available until	2	2		4

Generalize the Result to an N-Bit Comparator

C_1^0 and C_0^0 are available at time 2 (2 gate delays).*

C_1^1 and C_0^1 are available at time 4.

When are C_1^{N-1} and C_0^{N-1} available (these are the answer for an N-bit comparator)?

N-bit answer is available at time $2N$.

*In the notes, the inverters are counted, so paths from A and B are slightly longer, and all timings are increased by 1.

We May be Able to Improve Our Comparator Design

Can we do better?

(You should ask: better in what sense?)

Can we reduce delay?

- **Unlikely** with a bit-sliced design.
- Not easy to implement most functions with one gate.

Can we reduce area?

- **Maybe** ...
- Let's do some algebra.

Use Algebra to Find Common Subexpressions ($A'B$, AB')

Start with $Z_1 = AB' + AC_1 + B'C_1$

then use distributivity to pull out C_1 :

$$Z_1 = AB' + (A + B')C_1$$

and rewrite the $(A + B')$ factor as a NAND:


$$Z_1 = AB' + (A'B)'C_1$$

Similarly, $Z_0 = A'B + (AB)C_0$

Notice that we now reuse AB' and $A'B$.

The New Implementation Uses Fewer Gates

 The diagram below shows the new equations using NAND gates. $Z_1 = [(AB)'] ((A'B)C_1)'$
 The single-bit core is here. $= AB' + (A'B)C_1$




Area Heuristic for the New Design is 12

Let's analyze area for the new design.

How many literals? **6**

How many operators? **6 (NAND)**

 


Delay Analysis for the New Design

A to Z_1 : 3 gate delays (ignoring NOT)

C_1 to Z_1 : 2 gate delays

50% slower?!


B to Z_1 : 3 gate delays

 

Calculate the Time at Which C^M Becomes Available

When available?

When available?

 

A More Detailed Version of Our Calculations

Grey is “not relevant,” and green is maximum (time at which Z_i is available).

(bit slice 0)	A	B	C_1	C_0
input available at	0	0	$-\infty$	$-\infty$
delay from input to Z_1	+3	+3	+2	
Z_1 not available until	3	3	$-\infty$	
delay from input to Z_0	+3	+3		+2
Z_0 not available until	3	3		$-\infty$

A More Detailed Version of Our Calculations

Grey is “not relevant,” and green is maximum (time at which Z_i is available).

(bit slice 1)	A	B	C_1	C_0
input available at	0	0	3	3
delay from input to Z_1	+3	+3	+2	
Z_1 not available until	3	3	5	
delay from input to Z_0	+3	+3		+2
Z_0 not available until	3	3		5

The Slice-to-Slice Paths are the Important Ones

C_1^0 and C_0^0 are available at time 3 (2 gate delays).*

C_1^1 and C_0^1 are available at time 5.

When are C_1^{N-1} and C_0^{N-1} available (these are the answer for an **N-bit** comparator)?

N-bit answer is available at time $2N+1$.

*In the notes, the inverters are counted, so paths from A and B are slightly longer, and all timings are increased by 1.

Overall: Much Better Area for Slightly More Delay

So the new design

- **reduces area by about 40%** (area $12N$ compared to area $20N$).
- **increases delay by 1** ($2N+1$ gate delays compared to $2N$ gate delays).

Can We Do Even Better?

Yes, but it's not as easy.

For example, we can design a slice

- that compares multiple bits of **A** and **B**.
- See Notes 2.4.6 for an example.

We can also solve the full **N-bit** problem.

In other words, trade **more human work and complexity for better area and delay**.