

## ECE 120: Introduction to Computing

### A Comparator for 2's Complement

## Comparing 2's Complement Is Different from Unsigned

Let's design a comparator for  
**2's complement** numbers.

Is the function the same as  
with **unsigned** (like addition)?

For **unsigned**, **1001 > 0101**.

**Is the same true with 2's complement?**

**No.**

Should we just start over?

## Start with the Sign Bits

Let's try a little harder first...

If we compare two non-negative numbers,  
◦ the approach IS the same.  
◦ Right?

Maybe we can just use some extra logic to  
handle the sign bits?

## Consider All Possible Combinations of Sign Bits

Let's make a table based on the sign bits:

$A_s$	$B_s$	interpretation	solution
0	0	$A \geq 0$ AND $B \geq 0$	use unsigned comparator
0	1	$A \geq 0$ AND $B < 0$	$A > B$
1	0	$A < 0$ AND $B \geq 0$	$A < B$
1	1	$A < 0$ AND $B < 0$	unknown

## Interpret 2's Complement as Unsigned

Remember our “simple” rule for translating **2's complement** bit patterns to decimal?

The pattern  $A = a_{N-1}a_{N-2} \dots a_1a_0$

has value  $V_A = -a_{N-1}2^{N-1} + a_{N-2}2^{N-2} + \dots + a_02^0$

Let  $A$  be negative ( $a_{N-1} = 1$ ).

Interpreted as **unsigned**, the same bits have value  $V_A + 2^N$ .\*

\*The statement is true by definition of 2's complement, actually.

## Negative Numbers Can be Compared Directly

**What happens if we feed two negative 2's complement numbers into our unsigned comparator?**

We compare  $V_A + 2^N$  with  $V_B + 2^N$ .

And we get an answer:  $<$ ,  $=$ , or  $>$ .

Let's say that we find  $V_A + 2^N < V_B + 2^N$ .

In that case,  $V_A < V_B$ , so **we have the right answer for 2's complement.**

The same result holds for other answers.

## We Need Special Logic for the Sign Bits

Now we can complete our table:

$A_s$	$B_s$	interpretation	solution
0	0	$A \geq 0$ AND $B \geq 0$	use unsigned comparator
0	1	$A \geq 0$ AND $B < 0$	$A > B$
1	0	$A < 0$ AND $B \geq 0$	$A < B$
1	1	$A < 0$ AND $B < 0$	use unsigned comparator

## Simply Flip the Wires on the Most Significant Bit

Can we just flip the wires on the sign bits?

**For  $A_s = 0$  and  $B_s = 1$ ,**

- we feed in  $A_{N-1} = 1$  and  $B_{N-1} = 0$ , and
- the unsigned comparator produces  $A > B$ .

**For  $A_s = 1$  and  $B_s = 0$ ,**

- we feed in  $A_{N-1} = 0$  and  $B_{N-1} = 1$ , and
- the unsigned comparator produces  $A < B$ .

**What about when  $A_s = B_s$ ?**

Flipping the bits then has no effect!

**Answers are also correct in those cases.**

## One Comparator with a Control Signal can Do Both

---

Can we use a single comparator to perform both kinds of comparisons?

Yes, if we

- add a control signal **S**
- to tell the comparator whether to do **unsigned** (**S=0**) or **2's complement** (**S=1**) comparison.

Simply **XOR'ing the most significant bits of A and B with S** suffices.

- This approach leverages flexibility in the problem to reduce the logic needed.
- Analyze the design to understand how it works.