

ECE 120: Introduction to Computing

Multiplexers (Muxes)

Task: Checking for a Lower-Case Letter

What if we also need logic to check whether an **ASCII** character is a lower-case letter.

In **ASCII**, 'a' is **1100001** (0x61),
 and 'z' is **1111010** (0x7A).

Recall that 'A' is **1000001** (0x41),
 and 'Z' is **1011010** (0x5A).

**Can we reuse our solutions
 for upper-case letters?
 Of course we can!**

Change C_5' to C_5 to Obtain $L(C)$ from $U(C)$

Let's again say that the **ASCII** character is in $C = C_6C_5C_4C_3C_2C_1C_0$.

By breaking up the truth table, we obtained


$$U(C) = C_6C_5'C_4'(C_3 + C_2 + C_1 + C_0) + C_6C_5'C_4(C_3' + C_2')(C_3' + C_1' + C_0')$$

But lower-case characters are only different from upper-case in C_5 , which is 1 instead of 0.

$$L(C) = C_6C_5C_4'(C_3 + C_2 + C_1 + C_0) + C_6C_5C_4(C_3' + C_2')(C_3' + C_1' + C_0')$$

Change Comparator Input to Calculate $L(C)$

Or just change the comparators' inputs.

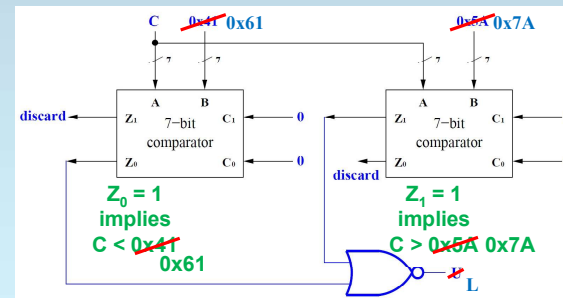

Want Logic to Choose Between Two Signals

What if we want one design to check for either upper-case or lower-case letters?

In a few examples,

- we added a control signal **S**
- to select between functions.

Can we design logic

- that uses a control signal **S** to select
- between two arbitrary signals, **D₁** (when **S = 1**) and **D₀** (when **S = 0**)?

Truth Tables for a 2-to-1 Multiplexer

A full truth table for such logic appears to the right.

But we could shorten it as shown below...

S	D ₁	D ₀	Q
0	x	0	0
0	x	1	1
1	0	x	0
1	1	x	1

Unselected inputs do not matter (marked with "x").

S	D ₁	D ₀	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

We Normally Use the Most Compact Truth Table

In this case, we can even write outputs in terms of other inputs, as shown here.

S	D ₁	D ₀	Q
0	x	0	0
0	x	1	1
1	0	x	0
1	1	x	1

Unselected inputs do not matter (marked with "x").

S	Q
0	D ₀
1	D ₁

Expression for a 2-to-1 Multiplexer

Let's solve with a K-map.

$$Q = S'D_0 + SD_1$$

		D ₁ D ₀			
		00	01	11	10
S	0	0	1	1	0
	1	0	0	1	1

S	D ₁	D ₀	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Expression for a 2-to-1 Multiplexer

But Q just selects D_0 or D_1 (as desired)!

$$Q = S'D_0 + SD_1$$


S	Q
0	D_0
1	D_1

Could we have just written this expression using the table to the right?

Q is D_0 when $S = 0$, and D_1 when $S = 1$...

Implementation and Symbolic Form of a 2-to-1 Mux

 The circuit below shows a **2-to-1 mux (multiplexer)**, for which the symbolic form appears to the right.




Selecting from More than Two Expressions

What if we want to select between four expressions, D_3 , D_2 , D_1 , and D_0 ?

One answer is to use muxes hierarchically:

 - start by using one 2-to-1 mux (signal S_1)
- to decide between D_3 or D_2 and D_1 or D_0 .




For the Second Level, Use More Muxes

But how do we deliver two expressions to each mux input?

Use more muxes (both controlled by S_0)!

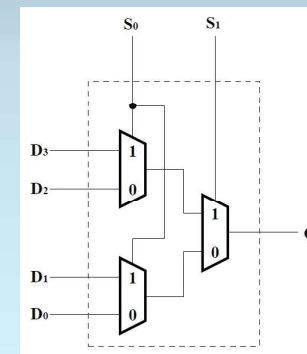
Notice that S_1S_0 then allows us to choose from four expressions.



AND Gates Represent Minterms ANDed with Data Inputs

For something as common as a mux, we typically build directly from gates.

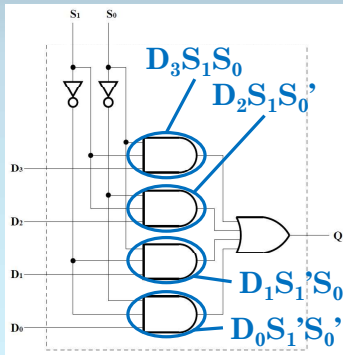Notice that **each AND gate produces a minterm of S_1, S_0 ANDed with the corresponding D_i .**




A 2^N -to-1 Mux Requires N Select Bits

The diagram to the right shows the **symbolic form of a 4-to-1 mux**.

We can, of course, further extend this idea to build 8-to-1 muxes, 16-to-1 muxes, and so forth.

 When selecting amongst $P = 2^N$ inputs $D_{P-1} \dots D_0$ we need N bits of select input, $S_{N-1} \dots S_0$.



Can Use Sets of Muxes to Select Amongst Groups of Bits

We can also generalize the idea of multiplexers by

- using a common control signal
- to select between groups of inputs.

Generally,

- **an N-to-M multiplexer**
- **represents M separate (N/M)-to-1 muxes**
- each with $\log_2(N/M)$ select bit inputs
- (typically $N/M = 2^K$ for some integer K).

Example of a Set of Muxes with Common Select Input

For example, recall the design of the **N-bit** adder and subtractor.

We could have used a **2N-to-N** mux

- to choose between B_i and B_i' for the adder's B input
- based on a common (one-bit) control signal S .

(Previously, we used the nature of the mux' data inputs, B_i versus B_i' , to simplify each mux' logic to an XOR gate.)

Another Design Problem: Checking Four Types of ASCII

Now think again about our **ASCII** checker.

Say that we want four kinds of comparison:

- control characters (0x00 to 0x1F),
- lower-case letters (0x41 to 0x5A),
- upper-case letters (0x61 to 0x7A), and
- digits (0x30 to 0x39).

How can we design logic to check for any of the four types?

The Answer? Use Muxes! Two 28-to-7 Muxes

