

ECE 120: Introduction to Computing

Another Example of Serialization: Power-of-2 Checker

Review of General Bit-Slice Model

General model parameters


N-bit operands

P bits of input from operands

Q bits of output produced

M bits between bit slices

 R bits of final output (not shown; produced by output logic operating on **M** bits from last bit slice).



Parameter Values for a Power-of-2 Checker

Power-of-2 checker parameters


N-bit operands

P = 2

Q = 0

M = 2

R = 1

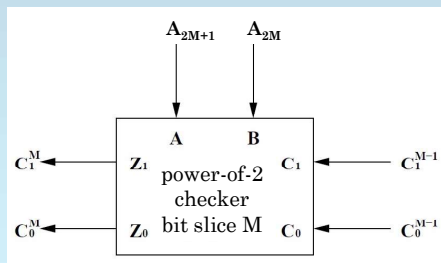

Initialization of a Power-of-2 Checker


Our power-of-2 checker bit slice uses the representation shown here to pass information between slices.

What values should be passed to the first bit slice?

No 1 bits yet, so $C_1 C_0 = 00$

C_1	C_0	meaning
0	0	no 1 bits
0	1	one 1 bit
1	0	not used
1	1	>one 1 bit

Example: A Power-of-2 Checker

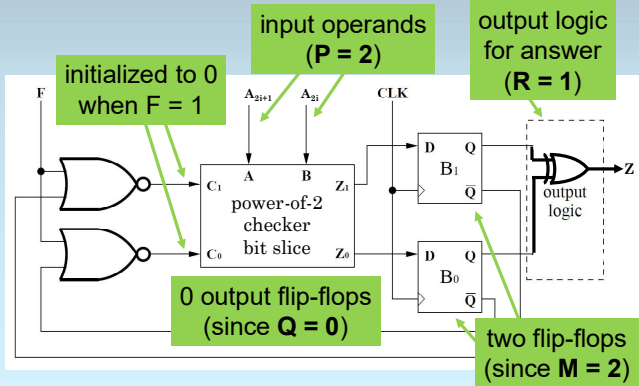

Discrete Time Implies Delayed Results: $N = 8$

yellow = inputs (green = bit slice labels)

cycle #	F	A	B	B_1	B_0	C_1	C_0	Z_1	Z_0
0	1	0	0	bits	bits	0	0	0	0
1	0	0	1	0	0	0	0	0	1
2	0	0	0	0	1	0	1	0	1
3	0	1	0	0	1	0	1	1	1
4	x	x	x	1	1	?	?	?	?

blue = outputs $Z = B_1 \oplus B_0 = 0$

A Power-of-2 Checker Consists of Four Parts

Let's analyze the area of a power-of-2 checker.

We have:


- one bit slice,
- two flip-flops,
- two 2-input NOR gates (selection logic),
- and a 2-input XOR.

16 2-input gates and four inverters

A Power-of-2 Checker Contains One Bit Slice

Here's our design for the power-of-2 checker bit slice.

 So we need **three 2-input gates** and **two 3-input gates**.



A Power-of-2 Checker Consists of Four Parts

Let's analyze the area of a power-of-2 checker.

We have:

- one bit slice,
- two flip-flops,
- two 2-input NOR gates (selection logic),
- and a 2-input XOR.

three 2-input gates
and two 3-input gates

16 2-input gates
and four inverters

Total: $3+16+2 = 21$ 2-input gates,
 $2 = 2$ 3-input gates,
 $4 = 4$ inverters, and
 1 2-input XOR.

Serial Design is Smaller for $N \geq 10$

To handle **N-bit** operands (2 bits per bit slice), a bit-sliced design requires:

- $3N/2$ 2-input gates (6N transistors),
- N 3-input gates (6N transistors), and
- 1 2-input XOR.


A serial design (independent of **N**) requires

- 21 2-input gates (84 transistors),
- 2 3-input gates (12 transistors),
- 4 inverters (8 transistors), and
- 1 2-input XOR.

The serial design is smaller for $N \geq 10$.

When Are Inputs Available?

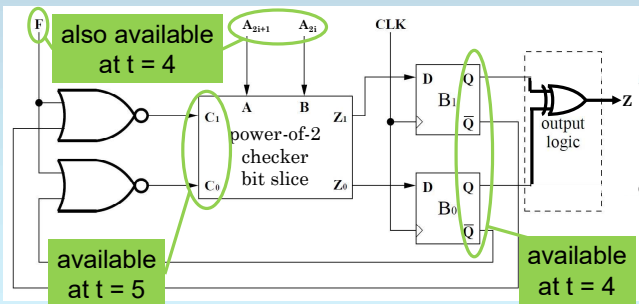
A rising edge arrives at $t = 0$ (gate delays).



Delay Analysis for the Bit Slice


And delay?

2 on all paths.

 

When Are Results Stored?

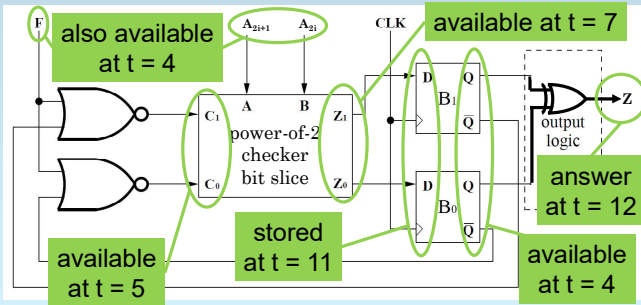A rising edge arrives at $t = 0$ (gate delays).



Serial Design is At Least 5.5x Slower

To handle **N-bit** operands, a bit-sliced design requires **$N + 1$ gate delays**.

For a serial design,

- the clock cycle must be **at least 11 gate delays**, and
- we must execute for **$N/2$ cycles**, so
- **N-bit** operands require **at least $11N/2$ gate delays**.

The serial design is at least ~5.5x slower.

(And may be even slower!)