

## ECE 120: Introduction to Computing

### Finite State Machines (FSMs)

## A Finite State Machine (FSM) Models a System

A model of a system

- system moves among a finite set of states
- motion based on external inputs
- produces external outputs

Examples include:

- coin/bill-operated machines,
- many vehicle control systems, and
- computers executing programs.

## An FSM Consists of Five Parts

1. a finite set of states (**bits**)
2. a set of possible inputs (**bits**)
3. a set of possible outputs (**bits**)
4. a set of transition rules (**Boolean expressions**)
5. methods for calculating outputs (**Bool. expr's**)

When implemented as a digital system, all parts of an FSM must be mapped to ... **bits!**

## A Digital FSM Must be Complete

We implement FSMs as clocked synchronous sequential circuits. (So state ID bits are stored in flip-flops.)

Given **any state** and **any combination of inputs**, a **transition rule** from the given state to a next state **must be defined**.

**Self-loops**—transitions from a state to itself—are acceptable.

## Use Keyless Entry as a Motivating Example

| meaning              | state    | driver's door | other doors | alarm on? |
|----------------------|----------|---------------|-------------|-----------|
| vehicle locked       | LOCKED   | locked        | locked      | no        |
| driver door unlocked | DRIVER   | unlocked      | locked      | no        |
| all doors unlocked   | UNLOCKED | unlocked      | unlocked    | no        |
| alarm sounding       | ALARM    | locked        | locked      | yes       |

Table is a **list of abstract states**.

## A List of Abstract States Need Only List States

In a list of abstract states,

- we can just list the states.
- Adding human meanings is optional (good to have if state names are generic).

Including outputs

- is also optional,
- and implies that **outputs depend only on state**.\*

\*An extra assumption that we will always make in our class.

## An Abstract Next-State Table Captures Expected Behavior

To specify transitions, we use a **next-state table**, which maps combinations of states and inputs into next states.

This is an **abstract next-state table**.

| state  | action/input  | next state |
|--------|---------------|------------|
| LOCKED | push "unlock" | DRIVER     |
| DRIVER | push "unlock" | UNLOCKED   |
| (any)  | push "lock"   | LOCKED     |
| (any)  | push "panic"  | ALARM      |

## Abstract Next-State Table Does Not Answer All Questions

We wrote transitions for typical use cases, but **the table can be incomplete, ambiguous, and even inconsistent**.

For example, what happens if the user pushes "lock" and "unlock" at the same time?

| state  | action/input  | next state |
|--------|---------------|------------|
| LOCKED | push "unlock" | DRIVER     |
| DRIVER | push "unlock" | UNLOCKED   |
| (any)  | push "lock"   | LOCKED     |
| (any)  | push "panic"  | ALARM      |

## Many Design Decisions are Usually Needed


All such **design decision questions should eventually be considered, and preferably answered.**

Be aware: **any digital logic implementation will define answers.**

Only when any possible answer is acceptable should you make use of “don’t cares.”

Typically, you should **review the final implementation** to determine how any questions left open are answered.
 
## Abstract State Transition Diagram: the Same Information



## It's Time to Make Our Design Complete and Concrete

The abstract next-state table and the abstract state transition diagram (can) **contain exactly the same information.**

They answer the same questions.

And **neither is complete.**

So. It's time for ... **bits!**

## Let's Start with the State Identifiers

**How many bits do we need to identify a state?**

There are 4 states.

$$\lceil \log_2(4) \rceil = 2 \text{ bits.}$$

Call them  $S_1S_0$ .

“S” is for “S(tate).”

## All Outputs and Inputs Must Also Use Bits

### What about outputs?

- D** driver door; 1 means unlocked
- R** remaining doors; 1 means unlocked
- A** alarm; 1 means alarm is sounding

### And inputs?

- U** unlock button; 1 means it's been pressed
- L** lock button; 1 means it's been pressed
- P** panic button; 1 means it's been pressed

## We Next Choose a Representation for States

Now we can choose a representation for states and rewrite our list of states.

The order of states in the list doesn't matter.

| <b>meaning</b>       | <b>state</b> | <b>S<sub>1</sub>S<sub>0</sub></b> | <b>D</b> | <b>R</b> | <b>A</b> |
|----------------------|--------------|-----------------------------------|----------|----------|----------|
| vehicle locked       | LOCKED       | 00                                | 0        | 0        | 0        |
| driver door unlocked | DRIVER       | 10                                | 1        | 0        | 0        |
| all doors unlocked   | UNLOCKED     | 11                                | 1        | 1        | 0        |
| alarm sounding       | ALARM        | 01                                | 0        | 0        | 1        |

## Choice of Representation Affects Amount of Logic Needed

As you may realize

- from your experience with bit-sliced designs,
- **the representation does matter** (for the amount of logic needed).

We will talk more later about ways to choose.

## Use $S_1^+S_0^+$ to Denote the Next State (in Next Clock Cycle)

The '+'s in  $S_1^+S_0^+$  indicate that these are values **in the next clock cycle**.

Let's rewrite the next-state table with bits.

- The table gives us  $S_1^+S_0^+$  as a function of current state  $S_1S_0$  and inputs **ULP**.
- Such tables typically use binary order for states (vertical) and inputs (horizontal).
- We use Grey code order on both axes for convenience (in copying to K-maps).

## How to Fill in the Next-State Table

Where should we start?

| current state<br>$S_1S_0$ | ULP |     |     |     |     |     |     |     |
|---------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
|                           | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00                        |     |     |     |     |     |     |     |     |
| 01                        |     |     |     |     |     |     |     |     |
| 11                        |     |     |     |     |     |     |     |     |
| 10                        |     |     |     |     |     |     |     |     |

What about multiple buttons?

Let's make some design decisions first...

## Completing the Design Requires Decisions

To fill in the next-state table

- starting with only the abstract design,
- we **need to make many design decisions**,
- including some that we haven't even recognized yet.

For example,

- What happens when the user presses more than one button?
- What happens when the user presses "unlock" in the **UNLOCKED** state?

## Make Design Decisions Early When Possible

Let's try to **make decisions first**.

**Design decisions** can shape the design, and **may conflict with one another**.

Making decisions early and writing them down ensures that

- any **issues are raised early**, and that
- **known decisions are not overlooked**
- (in which case the final design answers them implicitly, with no human guidance).

## Start by Deciding How to Handle Multiple Buttons

We're going to start by **prioritizing the buttons**.

Our rules:

- Panic has priority!
- Lock has second priority.
- Unlock only matters when neither of the others is pressed.

## Start with the Panic Button (Highest Priority)

The next-state table gives us  $S_1^+ S_0^+$ .

| current state<br>$S_1 S_0$ | ULP |     |     |     |     |     |     |     |
|----------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
|                            | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00                         | 01  | 01  |     |     | 01  | 01  |     |     |
| 01                         | 01  | 01  |     |     | 01  | 01  |     |     |
| 11                         | 01  | 01  |     |     | 01  | 01  |     |     |
| 10                         | 01  | 01  |     |     | 01  | 01  |     |     |

panic button pushed

## Continue with the Lock Button (Second Priority)

The next-state table gives us  $S_1^+ S_0^+$ .

| current state<br>$S_1 S_0$ | ULP |     |     |     |     |     |     |     |
|----------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
|                            | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00                         | 01  | 01  | 00  | 00  | 01  | 01  |     |     |
| 01                         | 01  | 01  | 00  | 00  | 01  | 01  |     |     |
| 11                         | 01  | 01  | 00  | 00  | 01  | 01  |     |     |
| 10                         | 01  | 01  | 00  | 00  | 01  | 01  |     |     |

lock button pushed

## No Buttons? No Change. All Self-Loops

What if the user pushes nothing?

| current state<br>$S_1 S_0$ | ULP |     |     |     |     |     |     |     |
|----------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
|                            | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00                         | 00  | 01  | 01  | 00  | 00  | 01  | 01  |     |
| 01                         | 01  | 01  | 01  | 00  | 00  | 01  | 01  |     |
| 11                         | 11  | 01  | 01  | 00  | 00  | 01  | 01  |     |
| 10                         | 10  | 01  | 01  | 00  | 00  | 01  | 01  |     |

no buttons pushed

## Finally, Unlock ... But are We Done?

Two transitions were defined for Unlock.

| current state<br>$S_1 S_0$ | ULP |     |     |     |     |     |     |     |
|----------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
|                            | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00                         | 00  | 01  | 01  | 00  | 00  | 01  | 01  | 10  |
| 01                         | 01  | 01  | 01  | 00  | 00  |     |     |     |
| 11                         | 11  | 01  | 01  | 00  | 00  |     |     |     |
| 10                         | 10  | 01  | 01  | 00  | 00  | 01  | 01  | 11  |

from DRIVER

## We Have More Design Decisions to Make!

What should happen if we press “unlock” when the car is already fully unlocked (in the **UNLOCKED** state)?

Maybe just stay **UNLOCKED**.

What should happen if we press “unlock” while the alarm is sounding?

- Continue to lock out an attacker / thief?
- Or open the doors so that the owner can climb inside quickly?

## Let's Implement Our Decisions

Ignore Unlock in both other cases.

| current state<br>$S_1S_0$ | ULP |     |     |     |     |     |     |     |
|---------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
|                           | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00                        | 00  | 01  | 01  | 00  | 00  | 01  | 01  | 10  |
| 01                        | 01  | 01  | 01  | 00  | 00  | 01  | 01  | 01  |
| 11                        | 11  | 01  | 01  | 00  | 00  | 01  | 01  | 11  |
| 10                        | 10  | 01  | 01  | 00  | 00  | 01  | 01  | 11  |

from ALARM (points to 101 column)

from UNLOCKED (points to 100 column)

## The Rest You Know How to Do


The rest is K-maps, expressions, and logic.

1. Express  $S_1^+$  and  $S_0^+$  in terms of  $S_1$ ,  $S_0$ ,  $U$ ,  $L$ , and  $P$ .
2. Express  $D$ ,  $R$ , and  $A$  in terms of  $S_1$ ,  $S_0$ .
3. Build the combinational logic.
4. Put the next state expressions  $S_1^+$  and  $S_0^+$  into the  $D$  inputs of two flip-flops.


You should do it as an exercise. Break up the truth tables or use 5-variable K-maps.
 
## One Last Tool: the Complete State Transition Diagram

The complete **state transition diagram** contains the information in both the state list and the next-state table.



## Complete State Transition Diagram

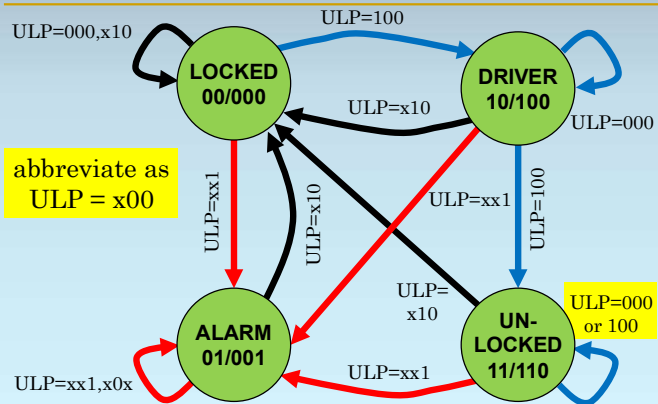

## Be Careful with Input Abbreviations

Input abbreviations can render a state transition diagram

- incomplete (if labels fail to cover all input combinations), or
- inconsistent (if labels indicate multiple next states).

For example,

- self-loop from **ALARM** labeled **ULP=xx1,x0x**:
- the patterns **x01** match both labels!
- In this case, these two combinations go to the same next state, so it's ok.