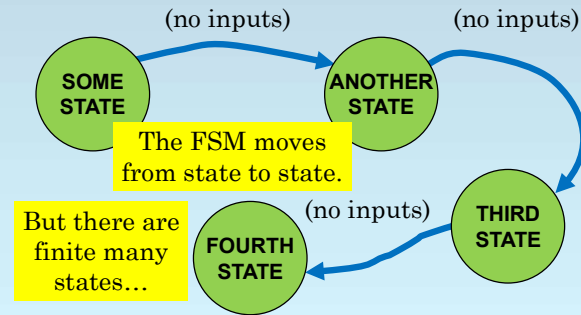



## An FSM with No Inputs Moves from State to State

What happens if an FSM has no inputs?


 
## Eventually, the States Form a Loop

So the FSM eventually returns to some state.



## A Counter Repeats a Loop of States (Forever)

An FSM without inputs is called a **counter**.

A counter may sometimes have inputs

- to start/stop the counter
- to reset the counter to a known state
- and sometimes to make the counter count in different ways (for example, up or down).

But the basic idea is the same: **the normal operation of a counter is a loop of states.**

## We Consider Both Synchronous and Ripple Counters

We focus mainly on

- **synchronous counters**, for which the flip-flops use a common clock signal.
- In other words, they are **clocked synchronous sequential circuits**, and allow us to pretend that time is discrete.

We will also look briefly at


- **ripple counters**, in which flip-flop outputs are used to clock other flip-flops.
- Such designs can save significant power.

## Example: 3-Bit Binary Counter

Let's do an example.

The state transition diagram to the right defines a 3-bit binary counter.

 
The states correspond to unsigned numbers 0 to 7, after which the counter returns to the 000 state.



## Write a Next-State Table

$S_2$	$S_1$	$S_0$	$S_2^+$	$S_1^+$	$S_0^+$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Start by writing a next-state table.

 

## Now Use K-Maps to Express the Next-State Values

Now copy into K-maps.

$S_2$	$S_1$	$S_0$	$S_2^+$	$S_1^+$	$S_0^+$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

$$S_0^+ = S_0' = S_0 \oplus 1$$

		$S_1 S_0$			
		00	01	11	10
$S_2^+$	0	1	0	0	1
	1	1	0	0	1

## Now Use K-Maps to Express the Next-State Values

$S_2$	$S_1$	$S_0$	$S_2^+$	$S_1^+$	$S_0^+$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Now copy into K-maps.

$$S_1^+ = S_1 S_0' + S_1' S_0$$

$$= S_1 \oplus S_0$$

		$S_1 S_0$			
		00	01	11	10
$S_1^+$	0	0	1	0	1
	1	0	1	0	1

## Now Use K-Maps to Express the Next-State Values

$S_2$	$S_1$	$S_0$	$S_2^+$	$S_1^+$	$S_0^+$
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Now copy into K-maps.

$$S_2^+ = S_2' S_1 S_0 + S_2 S_1' + S_2 S_0'$$

		$S_1 S_0$			
		00	01	11	10
$S_2^+$	0	0	0	1	0
	1	1	1	0	1

## When Do Place Values Change in Decimal Counting?

When you count in decimal,  
**when does a place value change?**

For example, when does the  
 number of thousands change?

**0999 → 1000    1999 → 2000    2999 → 3000**

What about the number of ten thousands?

**09999 → 10000    19999 → 20000    29999 → 30000**

Only **when the lower digits are all 9.**

## Can We Use Counting to Generalize the Counter Design?

So **what about in binary?**

**Only when the lower digits are all 1.**

We have ...

$$S_0^+ = S_0' = S_0 \oplus 1$$

$$S_1^+ = S_1 S_0' + S_1' S_0 = S_1 \oplus S_0$$

$$S_2^+ = S_2' S_1 S_0 + S_2 S_1' + S_2 S_0'$$

**Can you simplify the last equation?**

How about  $S_2^+ = S_2 \oplus (S_1 S_0)$ ?

## Use our General Formula to Build Bigger Counters

If you needed a 4-bit binary counter,

- do you need to draw a K-map?
- Or can you write  $S_3^+$  from our generalization?

$$S_3^+ = S_3 \oplus (S_2 S_1 S_0)$$

What about  $S_4^+$ ?


$$S_4^+ = S_4 \oplus (S_3 S_2 S_1 S_0)$$

And  $S_5^+$ ?

$$S_5^+ = S_5 \oplus (S_4 S_3 S_2 S_1 S_0)$$

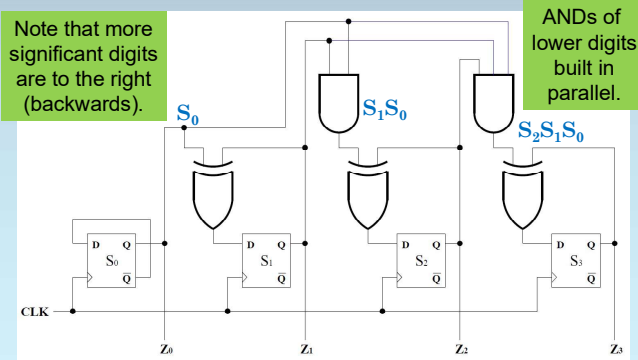
## Binary Counter with Parallel Gating

Note that more significant digits are to the right (backwards).


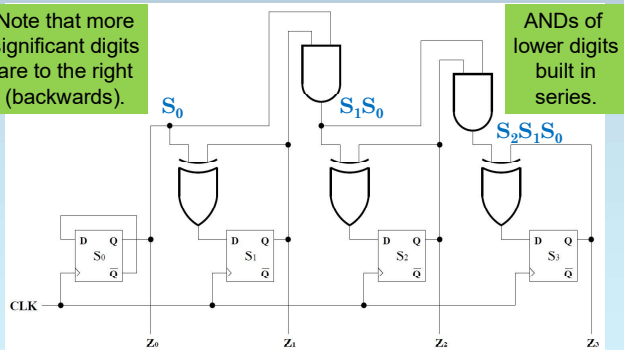
## Binary Counter with Serial Gating

Note that more significant digits are to the right (backwards).



## Comparing Serial and Parallel Gating

Parallel gating gives

- bigger gates (more area) and
- less delay.

Serial gating gives


- smaller gates (less area) but
- more delay.

In practice,

- gate sizes are limited, so
- counters use a combination of the two approaches.

## Flip-Flops in a Ripple Counter Do Not Share a Clock

We just designed a

 

Now, let's take a look at a **binary ripple counter**, in which the clock is not shared.

## Ripple Counters Require Less Power

In a ripple counter,

- **outputs from some flip-flops**
- **are used to clock other flip-flops** (used as the clock signal input).

Why?

- Recall that changing gate output values implies electric current, which implies power consumption.
- **Clocking flip-flops more slowly reduces energy consumption.**

## Ripple Counters are Slower

### What's the tradeoff?

Changes to internal state

- ripple through the counter from bit to bit, so
- they are **slower than synchronous counters**.

### What about clock skew?

In general, it may be an issue, but

- we will only **consider one simple design**, and
- more complex ripple counters can usually be designed in isolation from other logic.


## Binary Ripple Counters are Built from Bit Slices

The figure below shows a 4-bit binary ripple counter.

$S_i'$  is the clock input for  $S_{i+1}$ .

As you can see, the design uses a simple bit slice.

$S_i'$  is also the D input for  $S_i$ .

 

# A Timing Diagram Illustrates Counting

